

Today, we will:

- Do some more example problems and discussion about op-amp circuits
- Finish reviewing the pdf module: **op-amps (miscellaneous properties: GBP, CMRR)**

### Example: Op-amp circuits

**Given:** Consider the circuit shown.


\* Active, not passive because of the op-amp & feedback loop

(a) To do: What kind of circuit is this?

Active, inverting, low-pass filter/amplifier

(Low-pass (think about the capacitor))

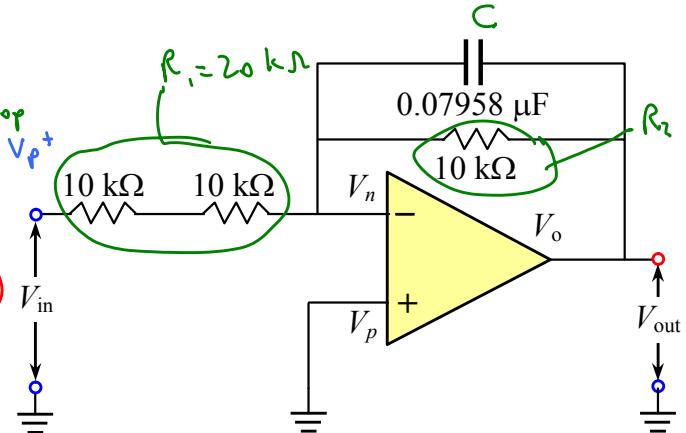(b) To do: Calculate the output voltage  $V_{out}$  when the input voltage is 2.0 V DC.



For a DC voltage input, the DC voltage charges up the capacitor; it acts like an open circuit after that

Circuit becomes an inverting amplifier with  $G = -\frac{R_2}{R_1} = -\frac{10}{20} = -0.5 = G_{amp}$

Thus,  $V_{out} = G_{amp} G_{filter} V_{in} = (-0.5)(1)(2.00 \text{ V}) = [-1.00 \text{ V DC}]$

(c) To do: Calculate the amplitude of the output voltage  $V_{out}$  when the input voltage is a pure sine wave with amplitude 1.0 V and frequency 200 Hz.

Since this is a low-pass filter/amplifier,  $f_{cutoff} = \frac{1}{2\pi R_2 C}$  [  $R_2$  is the resistor closest to the capacitor ]

$$f_{cutoff} = \frac{1}{2\pi(10,000\Omega)(0.07958 \times 10^{-6} \text{ F})} \left( \frac{\text{J} \cdot \text{A}}{\text{V}} \right) \left( \frac{\text{C}}{\text{V} \cdot \text{s}} \right) \left( \frac{\text{F} \cdot \text{V}}{\text{C}} \right) = 199.99 \text{ Hz}$$

(let's call it  $f_{cutoff} = 200 \text{ Hz}$ )

Overall gain,  $G_{overall} = G_{amplifier} \cdot G_{filter}$  [ The filter gain & the amplifier gain are multiplied together ]

In terms of amplitude,  $|G_{overall}| = |G_{amplifier}| \cdot |G_{filter}|$

(We use absolute value since we care only about the amplitude, not the sign)

$$|G_{overall}| = (0.5) \sqrt{1 + \left( \frac{f}{f_{cutoff}} \right)^2} = (0.5) \sqrt{1 + \left( \frac{200}{199.99} \right)^2} = 0.35355$$

$= 0.354$

$$\text{Finally, } |V_{out}| = \text{amplitude of output voltage} = |G_{overall}| |V_{in}| = (0.35355)(1.00 \text{ V}) = [0.354 \text{ V}]$$

Recall, from last lecture:

In general, we desire our electronic circuits to have **very low output impedance** and **very high input impedance**.


The input impedance of an inverting amplifier op-amp circuit is approximately  $R_1$ .

That is one reason why we generally want  $R_1$  to be large ( $> 1 \text{ k}\Omega$  as an absolute lower limit).

The output impedance of an inverting amplifier op-amp circuit is small, on the order of  $1 \Omega$ .


What about a *noninverting* amplifier? What are the input and output impedances?

### Inverting Amplifier:

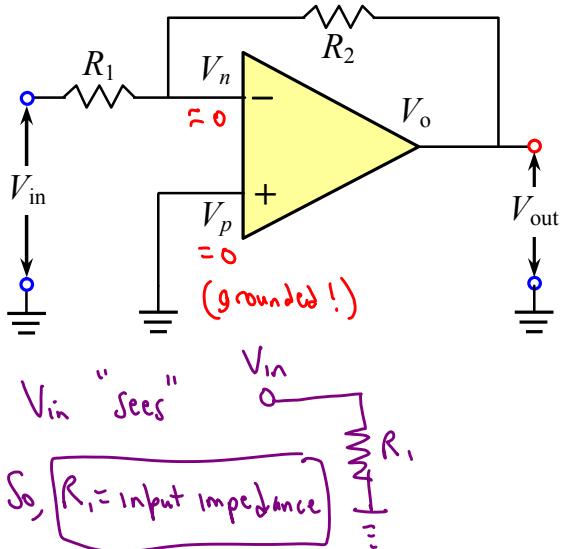

$R_1$  = Selected by user, & typically ranges from  $10 \text{ k}\Omega$  to  $100 \text{ k}\Omega$  (not real huge)

### Noninverting Amplifier:

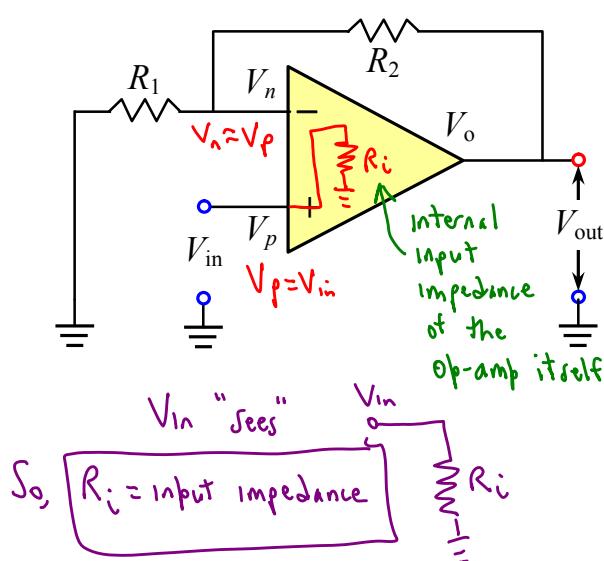

$R_i$  = Internal input impedance of the op-amp itself, which is typically tens of megohms (huge)

Bottom Line:

#### INVERTING AMPLIFIER:

- The input impedance of an inverting amplifier is  $\approx R_1$  (not real huge)
- The output impedance of an inverting amplifier is  $\approx 1 \Omega$  (small)

#### NONINVERTING AMPLIFIER:

- The input impedance of a noninverting amplifier is  $\approx R_i$  (huge, Mohms)
- The output impedance of a noninverting amplifier is  $\approx 1 \Omega$  (small)



Which is "better"?



- Noninverting is "better" if primary concern is input loading.
- Inverting is "better" if primary concern is noise, especially common mode noise.

Let's compare the amplification of **common mode noise** for *inverting* and *noninverting* amplifiers (common mode noise amplification).

*amplified common noise*

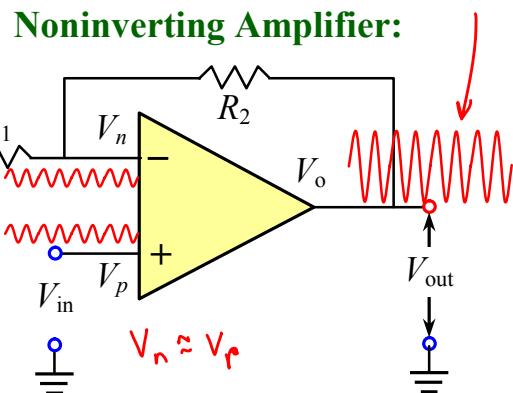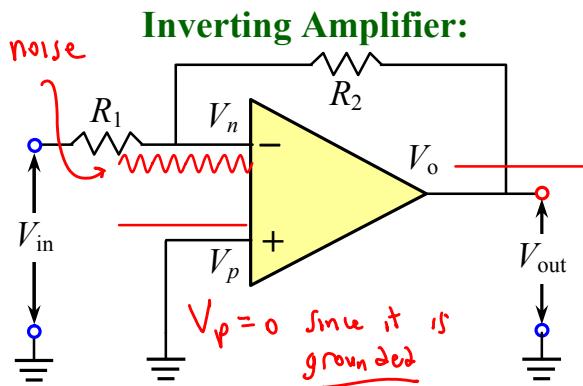

- $V_n$  may have noise, but  $V_p = 0$
- There is no common mode noise!

[Noise in  $V_{in}$  affects only  $V_n$ ]

- $V_n \approx V_p$ , so if there is noise in  $V_{in}$ , there is common mode noise in both  $V_n$  &  $V_p$
  - This common mode noise gets amplified by gain  $G_{cm}$  (common mode gain)
- [ $G_{cm}$  is an undesired property of the Op-amp]

- Comments:
- In both cases, signal & noise get amplified due to amplifier gain ( $G = -\frac{R_2}{R_1}$  for inverting &  $G = 1 + \frac{R_2}{R_1}$  for noninverting)
  - We are talking here about additional noise amplification due to  $G_{cm}$  effects



### Bottom Line:


- If *input loading* is of primary concern, noninverting amplifiers should be used.
- If *noise reduction* and *signal-to-noise issues* are of primary concern, inverting amplifiers should be used.

High-end audio equipment → noise is primary concern, so use inverting amplifiers
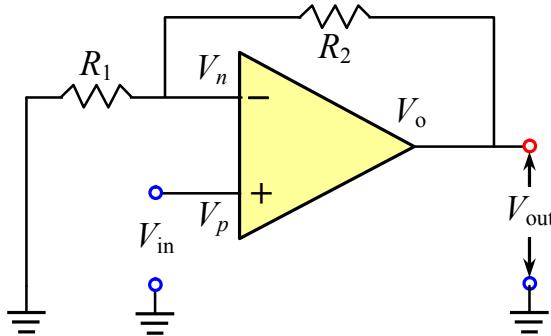
## Example: Op-amp circuits with GBP effects

**Given:** We need to amplify the output of a microphone (music converted into voltage) by a factor of 1000. We construct a noninverting amplifier as sketched, with:

- $R_1 = 1 \text{ k}\Omega$  (lower recommended limit)
- $R_2 = 999 \text{ k}\Omega$  (close to the upper recommended limit, which is  $1 \text{ M}\Omega$ )



**To do:**

(a) Calculate the *theoretical* gain of the circuit (at any frequency) if the op-amp were ideal.

(b) Calculate the *actual* gain for a type 741 op-amp, with GBP = 1.0 MHz at the following frequencies of the music:

- $f = 20 \text{ Hz}$  (lower limit of human hearing)
- $f = 261.63 \text{ Hz}$  (middle C → middle C on a piano is 261.626 Hz)
- $f = 4000 \text{ Hz} = 4 \text{ kHz}$  (a fairly high note)
- $f = 20 \text{ kHz}$  (upper limit of human hearing) (for healthy young people — older people lose their hearing, especially high freq.'s)

(c) Suggest a better circuit.

**Solution:**

$$(a) \text{ Noninverting amplifier} \rightarrow G_{\text{theory}} = 1 + \frac{R_2}{R_1} = 1 + \frac{999}{1} = 1000 = G_{\text{theory}}$$

(b). In real life, however, the actual  $G$  will be lower than this due to GBP effects.  
And, the reduction of  $G$  depends on the frequency component of the signal.

• Here, GBP = 1.0 MHz (given by op-amp specs)

• From the notes,

$$GBP_{\text{noninverting}} = G_{\text{theory}} \cdot f_c$$

( $f_c$  = internal cutoff frequency due to GBP effects)

(internal limitations of the op-amp)

$$f_c = \frac{GBP_{\text{inverting}}}{G_{\text{theory}}} = \frac{1,000,000 \text{ Hz}}{1000} = 1000 \text{ Hz}$$

The op-amp acts like a low-pass filter with

$$f_{\text{cutoff}} = f_c = 1000 \text{ Hz}!$$

$$G_{\text{actual}} = G_{\text{theory}} \cdot \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$= (1000) \frac{1}{\sqrt{1 + (20/1000)^2}} = 999.8$$

At  $f = 20 \text{ Hz}$ , GBP has very little effect;  $G \approx G_{\text{theory}}$

Repeat for all the frequencies in the signal:

$f$ (Hz)	$G_{\text{theory}}$	$G_{\text{actual}}$
20	1000	999.8
261.63	1000	967.4
4,000	1000	242.5
20,000	1000	49.9

We are losing amplification at the high frequencies!  
(The music would not sound so great)

(c) Better circuit? USE A TWO-STAGE AMPLIFIER (Two instead of one in series)

- Let  $G_1 = G_2 = \sqrt{1000} = 31.623$  since  $G = G_1 \cdot G_2$


- Pick  $R_1 = 2.00 \text{ k}\Omega$  (twice the lower recommended limit)

- Calculate  $R_2$  (remember that this is noninverting amplification)

$$G_1 = 1 + \frac{R_2}{R_1} \rightarrow R_2 = R_1(G - 1) = 2.00 \text{ k}\Omega (31.623 - 1) = 61.2455 \text{ k}\Omega$$

- So, for each (identical) stage, we  $R_1 = 2.00 \text{ k}\Omega \therefore R_2 = 61.2 \text{ k}\Omega$

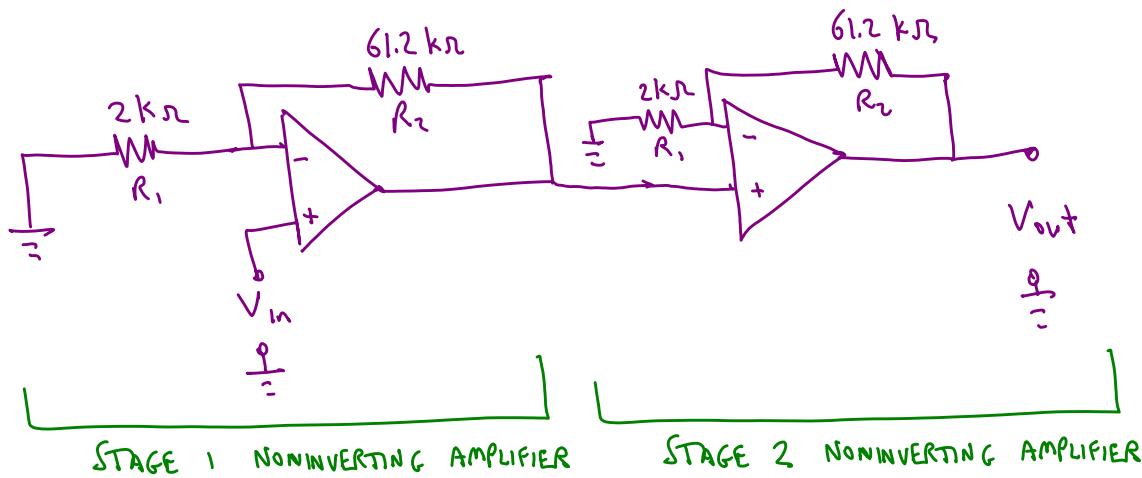- Revised two-stage noninverting amplifier circuit:



$$G_{\text{theory}} = 31.623$$

$$G_{\text{theory}} = 31.623$$

- Overall Theoretical gain =  $G_{\text{theory, overall}} = G_{\text{theory}_1} G_{\text{theory}_2} = 31.623^2 = 1000 \checkmark$


Now let's check the GBP effects for this revised 2-stage circuit:

For one stage,  $G_{\text{theory}} = 31.62$

$$f_c = \frac{\text{GBP}_{\text{nominating}}}{G_{\text{theory}}} = \frac{1.00 \times 10^6 \text{ Hz}}{31.62} = 31.62 \text{ kHz}$$

Notice how much larger is  $f_c$  now (31.62 kHz) compared to previously (previous  $f_c$  was 1000 Hz = 1.00 kHz)

Bode plot :

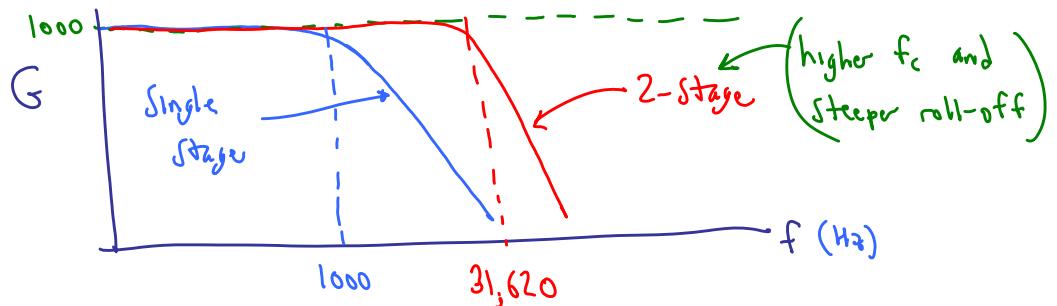

We say that the two-stage amplifier has a greater bandwidth

Re-do the table of actual gain. Here  $G_{\text{overall}} = (G_{\text{theory}})^2 (G_{\text{GBP}})^2$

Since there are 2 stages in series

$$\text{e.g., } @ f = 4000 \text{ Hz, } G_{\text{overall}} = (31.62)^2 \left[ \frac{1}{\sqrt{1 + \left( \frac{4000}{31620} \right)^2}} \right]^2 = 984.2$$

$f$ (Hz)	$G_{\text{theory}}$	$G_{\text{actual}}$
20	1000	$\approx 1000$
261.63	1000	999.9
4,000	1000	984.2
20,000	1000	714.3

(was 49.9 for the single-stage amplifier)

We still lose some amplitude at the very highest frequencies, but this music will sound much better!

Lesson:

Use a 2-stage amplifier to avoid GBP filtering effects  $\star$

### Example: Op-amp circuits

**Given:** We need to build an amplifier with a theoretical gain of 25 (or -25 – sign does not matter). We use a 741 op-amp with GBP = 1.0 MHz (1000 kHz). The resistors we have on hand are 5 kΩ, 10 kΩ, 20 kΩ, 50 kΩ, 100 kΩ, and 200 kΩ (we have several of each).

**(a) To do:** Draw an electrical circuit that will generate the required gain using a non-inverting amplifier. Repeat for an inverting amplifier.


**Solution:**

Non-inverting:

$$G_{\text{theory}} = 1 + \frac{R_2}{R_1} = 25$$

Pick  $R_1 = 5 \text{ k}\Omega$


Solve  $R_2 = 125 \text{ k}\Omega$

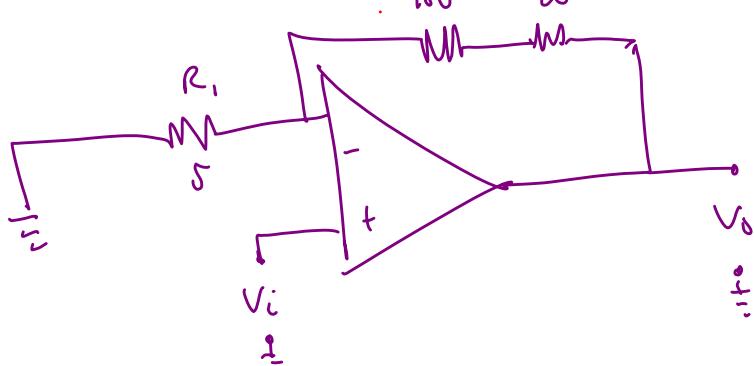

Inverting:

$$G_{\text{theory}} = -\frac{R_2}{R_1} \rightarrow R_2 = -R_1 G_{\text{theory}}$$

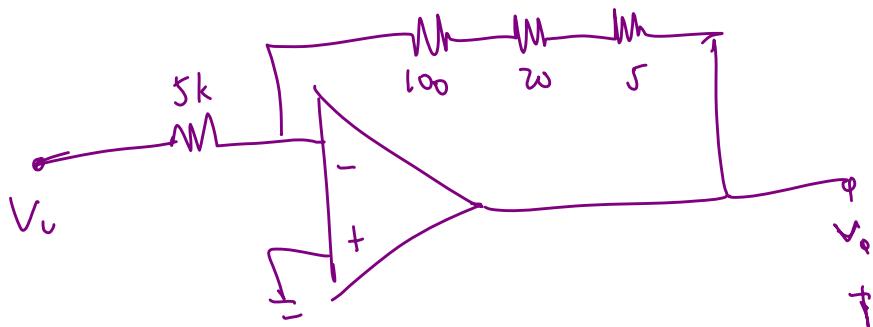Pick  $5 \text{ k}\Omega = R_1 \rightarrow R_2 = 125 \text{ k}\Omega$



★ Solve the rest of this problem on your own, for practice

**(b) To do:** For the non-inverting case, calculate the overall gain of the amplifier if the signal being amplified has a frequency of 20 kHz. Repeat for the inverting amplifier.

**Solution:**

Non-inverting:

ANSWERS:

$$f_c = 40 \text{ kHz}$$

$$G_{\text{overall}} = 22.4$$

Inverting:


$$f_c = 38.46$$

$$G_{\text{overall}} = -22.2$$

(c) To do: For the inverting case, suppose we split up the gain into two stages to reduce the effect of the GBP-filtering. Calculate the overall gain of the amplifier if the signal being amplified has a frequency of 20 kHz.

\* DO THIS ON YOUR OWN FOR PRACTICE

Solution:

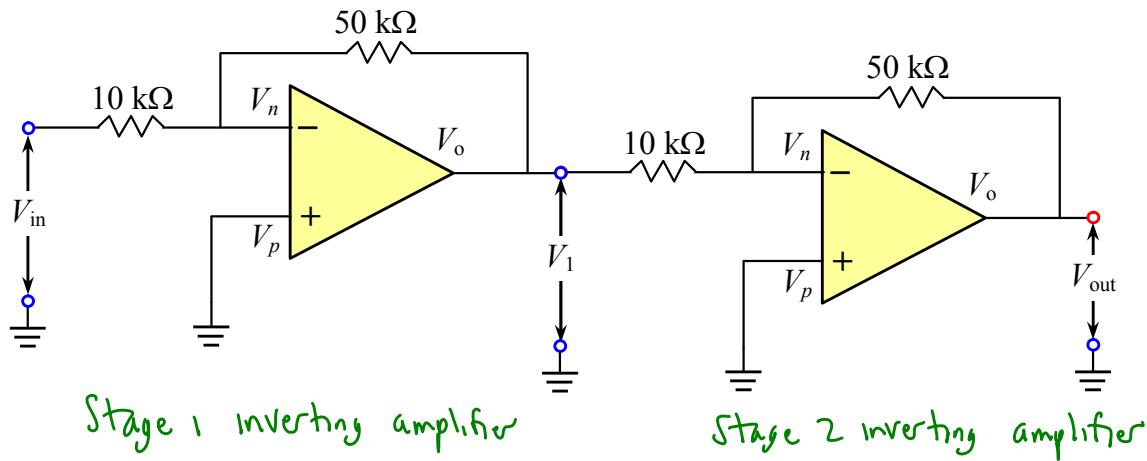

$$\text{Combined theoretical gain} = \underline{\underline{25}}$$

However, due to GBP effects, the actual overall gain is lower

$$f_c = 166.67 \text{ kHz}$$

$$G_{\text{overall}} = (-4.964)^2 = \boxed{24.6}$$

[GBP effects are not significant in this problem]