


Color organ – by Kevin Shadle, Spring 2009

From Wikipedia, the free encyclopedia

Jump to: [navigation](#), [search](#)

The term **color organ** refers to a tradition of mechanical (18th century), then electromechanical, devices built to represent sound or to accompany music in a visual medium—by any number of means. In the early 20th century, a silent color organ tradition (Lumia) developed. In the 60s and 70s, the term 'color organ' became popularly associated with electronic devices that responded to their music inputs with [light shows](#). The term '[light organ](#)' is increasingly being used for these devices; allowing 'color organ' to reassume its original meaning

DEPARTMENTS	Home > Kits > Color Organ Kits
Specials	120VAC 3 Channel Color Organ Kit
May / June - New Arrivals	
May / June - Sale Items	
May / June - \$1 Sale Special	
May / June - Blowout \$.50	
March / April Flyer	
March / April - New Arrivals	
FREE Gift Coupons	
Rare and Esoteric	
AC Items	
Adapters	
Alarms	
Assortments	
Audio Components	
Bags	
Batteries	
Breadboards	
Boxes / Cases	
Cables	
Capacitors	
Circuit Boards	
Coils / Inductors	
Computer Items	
Connectors	

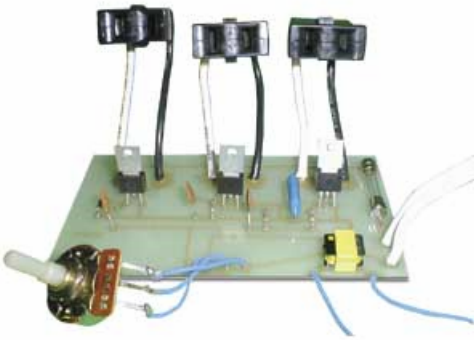


Item Number : C4530
Unit Price: \$15.95
Quantity
BUY NOW **ADD TO WISH LIST**

[Refer this page to a friend](#)

Detailed Description

Very popular 3 channel color organ causes lights of your choice (up to 200 watts per channel) to flash to the beat and frequency of the music. Simply connect the color organ to your stereo speaker. Has input transformer to isolate color organ from stereo and has 3 different signal filtering stages for low, medium and high notes. Kit features level control and 3 separate AC outlets to connect Christmas lights, lamps, etc.

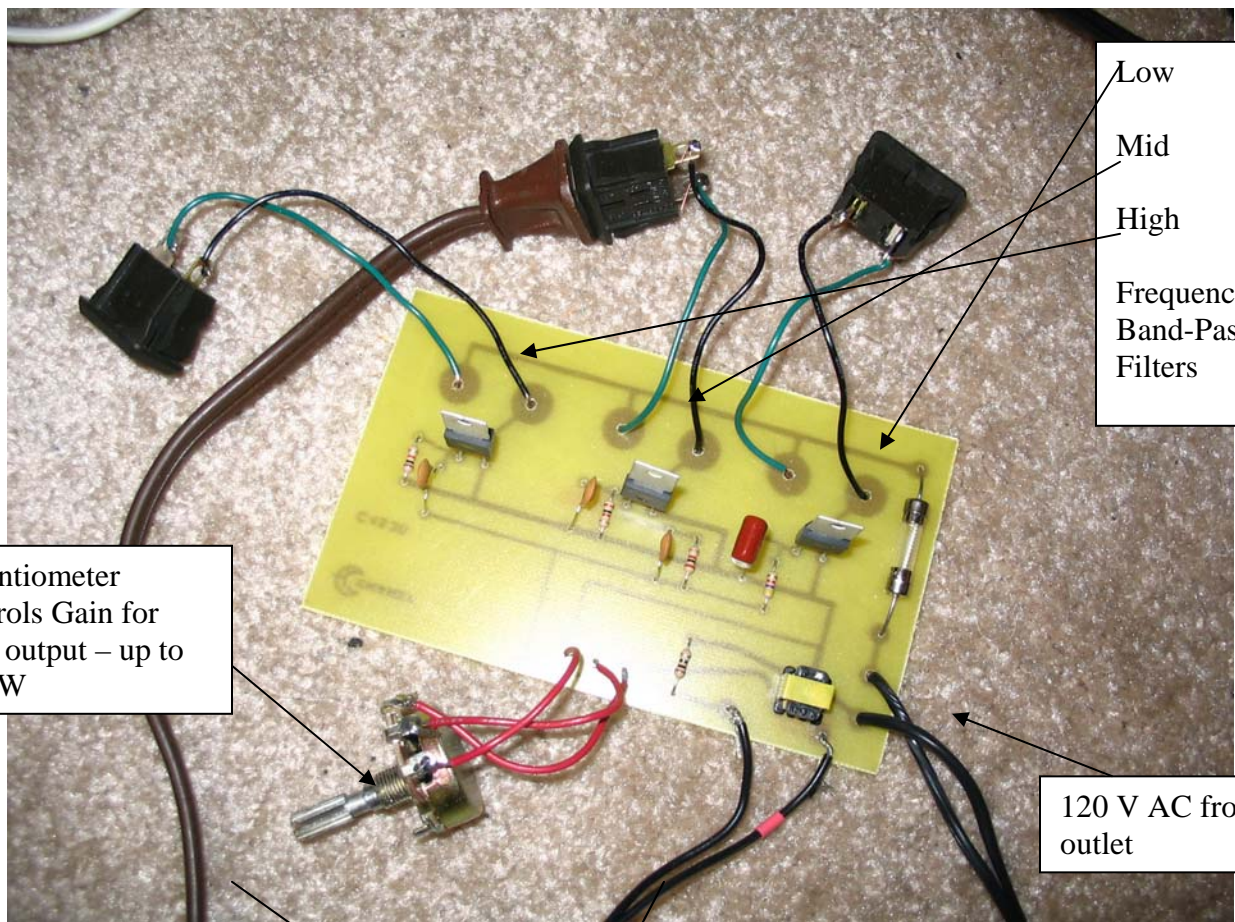

Low
Mid
High
Frequency
Band-Pass
Filters

Potentiometer
controls Gain for
total output – up to
600 W

120 V AC from
outlet



Audio Output from 1 channel
of 4-sprkr surround sound.

How this relates to course material:




Blacklights (40W) total
powered from mid-range
audio frequency.

The color organ has 3 different filters that allow a low (low pass filter), mid-range (band-pass filter), and high-range (high-pass filter) frequency to 3 different channels. The voltage at each of these channels can be connected to the positive and negative terminals of lights (I used blacklights), lamps, or anything with an AC drive.

A rotary potentiometer is also included in the kit, which adjusts the voltage connected to the input of the 3 channels to add sensitivity to the brightness of the lights. This voltage will be $V_{out} = V_{in} (x/L)$ or (θ_1/θ_2) because it is angular displacement.

This demonstrates visually how the signal from an audio source (one channel from my surround sound system – which is another set of filters itself) can be filtered into 3 different categories (low, mid, and high) for the audible frequencies (100 Hz, 1000 Hz, 5000 Hz roughly). Also, the potentiometer shows how the gain can be adjusted equally to all three channels.

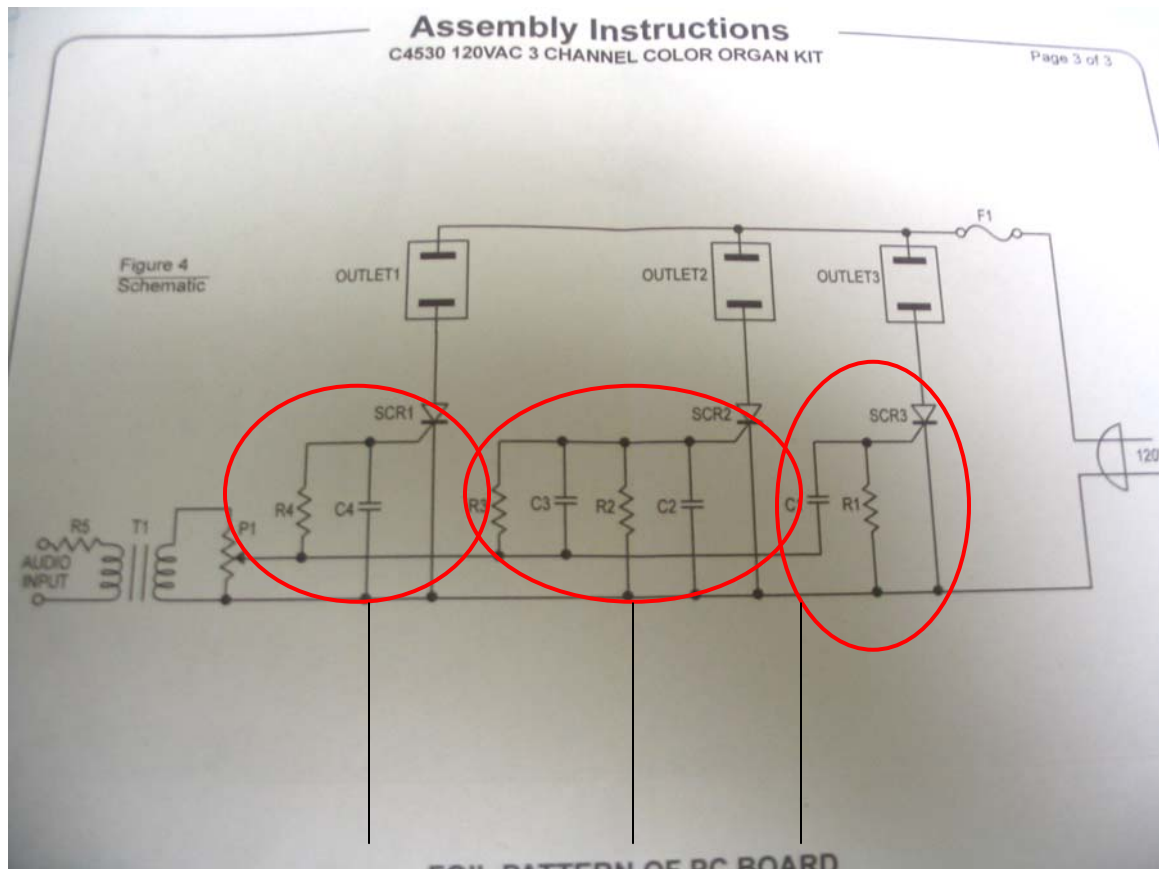This is the **schematic** that came with the circuit board to show where to solder components.



As shown in the lecture slides, these are good examples of a low-pass, band-pass, and high pass filter from left to right. Note: the band-pass combines both low and high – showing 2 capacitors.