## M E 345

#### Today, we will:

- Do some example problems Filters
- Review the pdf module: Digital Filters

## **Example: Low-pass filter circuit**

**Given**: The following components are available:

• two resistors,  $10.0 \text{ k}\Omega$  and  $87.0 \text{ k}\Omega$ 

• a capacitance decade box

The input voltage contains a signal frequency of 50 Hz, and some unwanted noise at 1000 Hz. We want to amplify the signal, with  $G_{\text{amplifier}} \approx 8.5$ , and we decide to use a first-order low-pass filter with a cutoff frequency of 200 Hz to attenuate the noise.

(a) To do: Draw the filter circuit and calculate the required capacitance.

# Solution:

(*b*) **To do**: Calculate the overall gain of both the signal and the noise, and calculate how well we have improved the signal-to-noise ratio (SNR). *Note: SNR is the ratio of signal power to noise power.* Since electrical power is proportional to voltage<sup>2</sup>, we define SNR as



Solution:

## **Example: Digital data acquisition and Filters**

**Given:** A voltage signal has a frequency around 100 Hz, and ranges from 5.0 to 6.0 volts. There is also some unwanted AC noise at a frequency around 5000 Hz, with an amplitude of  $\pm 0.005$  V. The digital data acquisition system is 12-bit, and has a range from -5 to 5 volts.

(*a*) To do: Calculate an appropriate DC offset and gain in order to utilize the full range of the A/D system.

Solution: DC offset = V, Gain = Schematic diagram of the circuitry:



(b) To do: Design a first-order filter with these requirements:

- Use resistors and capacitors only
- Don't attenuate the 100 Hz signal by more than 25% (after the gain).
- Attenuate the 5000 Hz noise to lower than the quantizing error of the A/D system (in other words, remove it completely, since its amplitude will be reduced to the noise level of the A/D converter).

#### Solution: