

**Today, we will:**


- Do some more example problems and discussion about op-amp circuits
- Finish reviewing the pdf module: **op-amps (miscellaneous properties: GBP, CMRR)**

**Example: Op-amp circuits**

**Given:** Consider the circuit shown.

**(a) To do:** What kind of circuit is this?

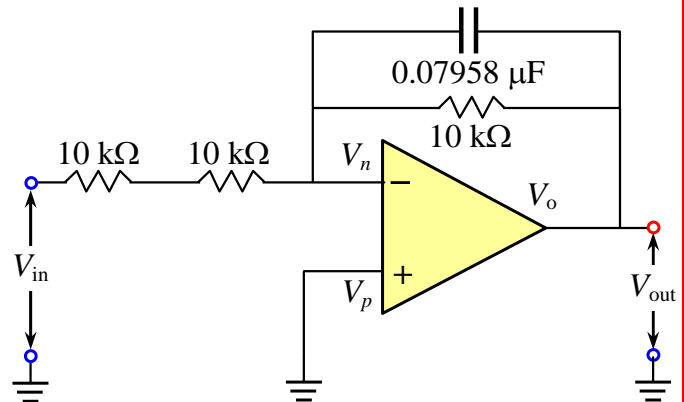**(b) To do:** Calculate the output voltage  $V_{out}$  when the input voltage is 2.0 V DC.



**(c) To do:** Calculate the amplitude of the output voltage  $V_{out}$  when the input voltage is a pure sine wave with amplitude 1.0 V and frequency 200 Hz.

Recall, from last lecture:

In general, we desire our electronic circuits to have *very low output impedance* and *very high input impedance*.


The input impedance of an inverting amplifier op-amp circuit is approximately  $R_1$ .

That is one reason why we generally want  $R_1$  to be large ( $> 1 \text{ k}\Omega$  as an absolute lower limit).


The output impedance of an inverting amplifier op-amp circuit is small, on the order of  $1 \Omega$ .

What about a *noninverting* amplifier? What are the input and output impedances?

**Inverting Amplifier:**

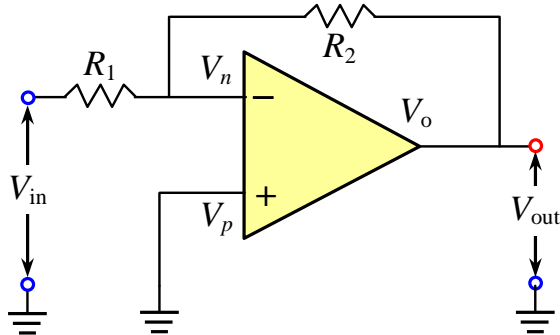


**Noninverting Amplifier:**

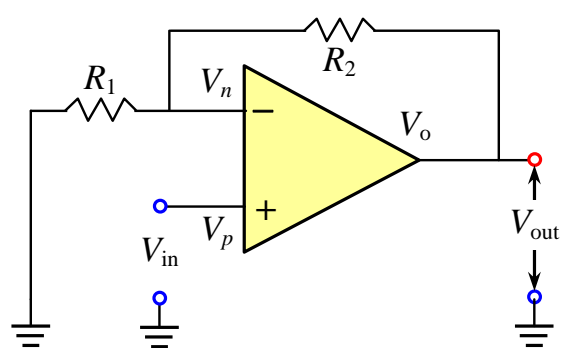


Let's compare the amplification of **common mode noise** for *inverting* and *noninverting* amplifiers (common mode noise amplification).

### Inverting Amplifier:

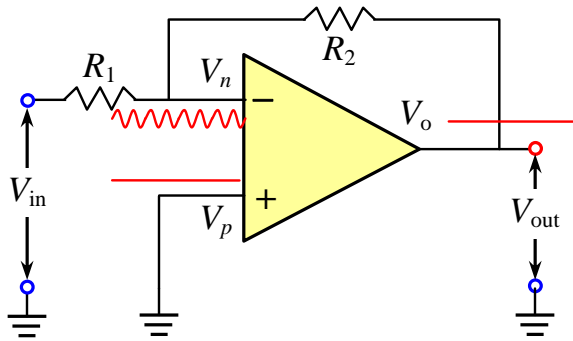

### Noninverting Amplifier:

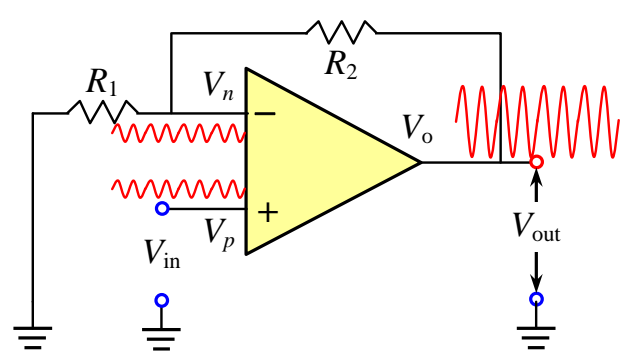


### Bottom Line:

- If *input loading* is of primary concern, *noninverting* amplifiers should be used.
- If *noise reduction* and *signal-to-noise* issues are of primary concern, *inverting* amplifiers should be used.
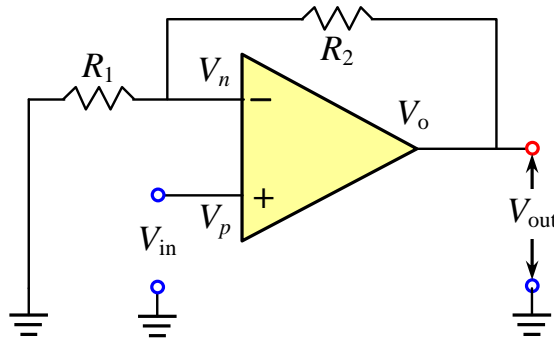
### Example: Op-amp circuits with GBP effects

**Given:** We need to amplify the output of a microphone (music converted into voltage) by a factor of 1000. We construct a noninverting amplifier as sketched, with:

- $R_1 = 1 \text{ k}\Omega$
- $R_2 = 999 \text{ k}\Omega$



#### To do:

(a) Calculate the *theoretical* gain of the circuit (at any frequency) if the op-amp were ideal.  
(b) Calculate the *actual* gain for a type 741 op-amp, with  $\text{GBP} = 1.0 \text{ MHz}$  at the following frequencies of the music:

- $f = 20 \text{ Hz}$  (lower limit of human hearing)
- $f = 261.63 \text{ Hz}$  (middle C)
- $f = 4000 \text{ Hz} = 4 \text{ kHz}$  (a fairly high note)
- $f = 20 \text{ kHz}$  (upper limit of human hearing)

(c) Suggest a better circuit.

#### Solution:

### Example: Op-amp circuits

**Given:** We need to build an amplifier with a theoretical gain of 25 (or -25 – sign does not matter). We use a 741 op-amp with  $\text{GBP} = 1.0 \text{ MHz}$  (1000 kHz). The resistors we have on hand are  $5 \text{ k}\Omega$ ,  $10 \text{ k}\Omega$ ,  $20 \text{ k}\Omega$ ,  $50 \text{ k}\Omega$ ,  $100 \text{ k}\Omega$ , and  $200 \text{ k}\Omega$  (we have several of each).

**(a) To do:** Draw an electrical circuit that will generate the required gain using a non-inverting amplifier. Repeat for an inverting amplifier.

**Solution:**

Non-inverting:

Inverting:

**(b) To do:** For the non-inverting case, calculate the overall gain of the amplifier if the signal being amplified has a frequency of 20 kHz. Repeat for the inverting amplifier.

**Solution:**

Non-inverting:

Inverting:

**(c) To do:** For the inverting case, suppose we split up the gain into two stages to reduce the effect of the GBP-filtering. Calculate the overall gain of the amplifier if the signal being amplified has a frequency of 20 kHz.

**Solution:**

