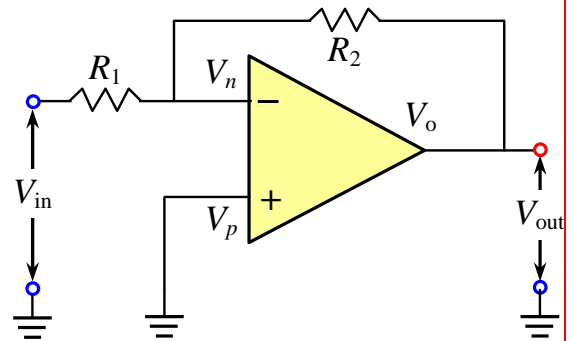


Today, we will:

- Do another example problem – op-amps with GBP effects.
- Begin the pdf module: **Stress, Strain, and Strain Gages**, and do some examples.

Example: Op-amp circuit with GBP effects

Given: Ben amplifies the voltage output of a microphone by a factor of 1000 using an inverting amplifier as sketched, with $R_1 = 1.00 \text{ k}\Omega$ and $R_2 = 1.00 \text{ M}\Omega$. The quality of the amplified music sounds odd to Ben, particularly at high frequencies, but he is clueless as to why this is happening. His friend Ashley took M E 345 and remembers something about GBP effects with op-amps. She looks up the specs for Ben's op-amp: $\text{GBP}_{\text{noninverting}} = 0.450 \text{ MHz}$. She explains to Ben that his op-amp is acting like a first-order low-pass filter, and that is why he is losing some of the high frequencies in his music.



**To do:**

- Calculate the internal cutoff frequency of this op-amp circuit.
- Compare the *theoretical* gain and the *actual* gain of this circuit at $f = 10,000 \text{ Hz}$.

Solution:

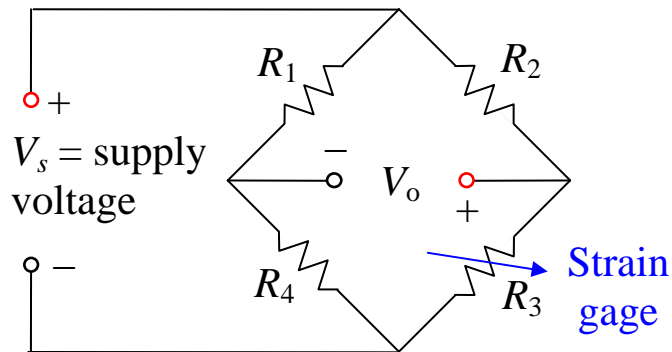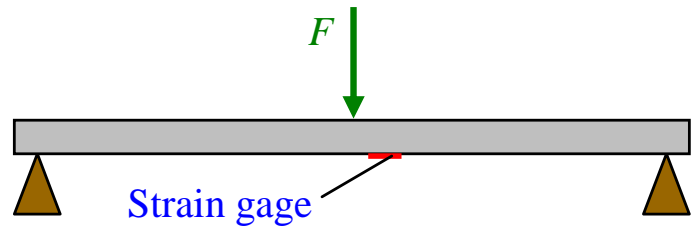Example: Strain gages

Given: We are measuring the strain on the surface of a beam. The beam's modulus of elasticity is $E = 193 \text{ GPa}$. We use one strain gage on the bottom of the beam, as shown; the strain gage factor is $S = 2.02$. We construct a quarter bridge Wheatstone bridge circuit, with the strain gage on resistor 3, as sketched below. All resistors, including the strain gage itself (when unloaded) are 120Ω . The supply voltage is 5.00 V DC , and the bridge is initially balanced when there is no load.



(a) To do: Will V_o be positive or negative when a downward load is added?

Solution:

Recall from the pdf notes:

$$\frac{V_o}{V_s} \approx \frac{R_{2,\text{initial}} R_{3,\text{initial}}}{(R_{2,\text{initial}} + R_{3,\text{initial}})^2} \left(\frac{\delta R_1}{R_{1,\text{initial}}} - \frac{\delta R_2}{R_{2,\text{initial}}} + \frac{\delta R_3}{R_{3,\text{initial}}} - \frac{\delta R_4}{R_{4,\text{initial}}} \right)$$

(b) To do: For a loading in which $V_o = 1.25$ mV, calculate the strain ε_a in units of microstrain.


Solution:

(c) To do: If the material is cold work tool steel with modulus of elasticity $E = 193 \text{ GPa}$ (at room temperature), calculate the axial stress (in MPa) in the beam under this load.

Solution:

(d) To do: Suppose we want more sensitivity, so we glue another strain gage on *top* of the beam. Which resistor should we use for this second active strain gage?

Solution:

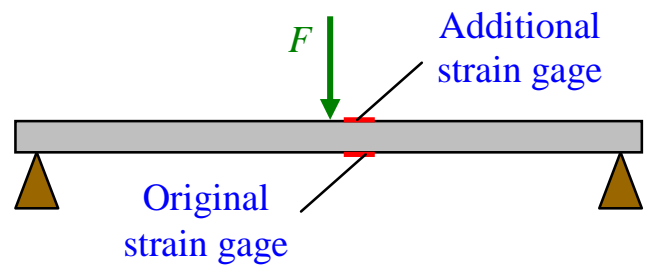

Again from the pdf notes:

$$\frac{V_o}{V_s} \approx \frac{R_{2,\text{initial}} R_{3,\text{initial}}}{(R_{2,\text{initial}} + R_{3,\text{initial}})^2} \left(\frac{\delta R_1}{R_{1,\text{initial}}} - \frac{\delta R_2}{R_{2,\text{initial}}} + \frac{\delta R_3}{R_{3,\text{initial}}} - \frac{\delta R_4}{R_{4,\text{initial}}} \right)$$

(e) To do: For the setup of Part (d) with the same strain as in Part (b), calculate output voltage V_o .

Solution: