Profe

Professor John M. Cimbala

Lecture 28

Today, we will:

M E 345

- Discuss how to compensate for strain gages with long lead wires
- Do a review example problem A/D converters, op-amps, filters, and strain gages

Example: Strain gage with long lead wires – how to compensate

Given: A quarter-bridge strain gage circuit is constructed with 120- Ω resistors and a 120- Ω strain gage as usual. The main problem here is that the experiment is very far away – the lead wires going to the strain gage are 40 ft long, and the lead wires have a resistance of 0.026 Ω per foot. The lead wire resistances can lead to problems since R_{lead} changes with temperature.



To do: Devise a modified circuit that will cancel out the effect of the lead wires. **Solution**: A clever "trick", using 3 wires connected to the strain gage rather than just 2:



Recall the approximate equation for V_0 when all four resistors of the Wheatstone bridge have small changes in resistance:

$$\frac{V_{o}}{V_{s}} \approx \frac{R_{2,\text{initial}}R_{3,\text{initial}}}{\left(R_{2,\text{initial}} + R_{3,\text{initial}}\right)^{2}} \left(\frac{\delta R_{1}}{R_{1,\text{initial}}} - \frac{\delta R_{2}}{R_{2,\text{initial}}} + \frac{\delta R_{3}}{R_{3,\text{initial}}} - \frac{\delta R_{4}}{R_{4,\text{initial}}}\right)$$

Another way to draw this same circuit, to aid in understanding it:



Example: Strain gages and digital data acquisition [a comprehensive review problem] Given: A quarter-bridge Wheatstone bridge circuit is used with a strain gage to measure strains up to $\pm 1000 \ \mu$ strain for a beam vibrating at a maximum frequency of 50 Hz.

- the supply voltage to the Wheatstone bridge is $V_s = 5.00 \text{ V DC}$
- all Wheatstone bridge resistors and the strain gage itself are 120 Ω
- the circuit is initially balanced at zero strain
- the strain gage factor for the strain gage is S = 2.04
- there is some unwanted noise in output V_0 : $f_{\text{noise}} = 3600 \text{ Hz}$ and amplitude = $\pm 0.50 \text{ mV}$
- the output voltage V_0 is sent into a 12-bit A/D converter with a range of $\pm 5 \text{ V}$
- op-amps, resistors, and capacitors are available in the lab
- all op-amps have a GBP (noninverting) of 1.2 MHz

To do: Design a circuit with the highest possible resolution (i.e., a circuit that utilizes the full range of the A/D converter), and minimizes the noise.

Solution:

First, we calculate $V_{o,max}$ = max voltage output from the strain gage circuit:

$$V_{o, \max} = V_s \varepsilon_a \frac{n}{4} S = (5.00 \text{ V})(1000 \times 10^{-6}) \frac{1}{4} (2.04) = 2.55 \times 10^{-3} \text{ V}$$

Thus, V_0 varies between -2.55 mV and +2.55 mV. Now, to utilize the full range of the A/D converter, we need to amplify by a factor of

$$G = \frac{\pm 5.00 \text{ V}}{\pm 2.55 \times 10^{-3} \text{ V}} = \pm 1960.78 \text{ [sign depends on type of amplifier]}$$

We suggest this circuit (single stage inverting amplifier) as a starting point:



To achieve the required gain, we would use, say, $R_{1, \text{ op-amp}} = 1 \text{ k}\Omega$, and $R_{2, \text{ op-amp}} = 1.96 \text{ M}\Omega$. Questions:

1. Why do we ground the Wheatstone bridge at V_0^- instead of at the bottom of the bridge?

2. Why did we put a buffer between the Wheatstone bridge and the amplifier?

3. Why are we using an *inverting* (rather than a noninverting) amplifier?

4. To get positive V_{out} when the strain is positive, which resistor should be the strain gage?

- 5. Why is this circuit not so great, and what should we do to improve it? **Answers**:
 - $R_{1, \text{ op-amp}} = 1 \text{ k}\Omega$ is at the lower recommended limit (not so great input impedance)
 - $R_{2, \text{ op-amp}}$ exceeds the recommended 1 M Ω limit (leads to stray capacitance effects)
 - G is huge, and can lead to GBP effects as discussed previously
 - To improve this circuit, let's instead constructy a *two-stage amplifier*:



In this case, we can choose better values of the op-amp resistors. Namely, the gain of each amplifier is the square root of the total gain, i.e.,

$$G_{\rm stage} = -\sqrt{1960.78} = -44.281$$

so we choose, for example, $R_{1, \text{ op-amp}} = 10.0 \text{ k}\Omega$, and $R_{2, \text{ op-amp}} = 442.8 \text{ k}\Omega$.

Questions:

1. To get positive V_{out} when the strain is positive, which resistor should be the strain gage?

2. What should we add to get rid of the high frequency (3600 Hz) noise?