

Today, we will:

- Do a review example problem – filters and digital data acquisition
- Begin to review the pdf module: **Operational Amplifiers (Op-Amps)**, and do examples
- Discuss some additional items not in the pdf notes about op-amps

Example: Digital data acquisition and filters

Given: Annalee is testing an electronics circuit in the lab. There is some pesky high frequency noise at around 3600 Hz with an amplitude around ± 0.3 V. She uses a 12-bit A/D converter to sample data from the circuit. The data acquisition system is set up with a range of -10 to 10 V, and she builds a low-pass filter to filter out the high frequency noise.

To do:

- Calculate the gain (G) necessary to attenuate the 3600 Hz noise to a level that is below the quantizing error of the A/D converter.
- Annalee builds a passive first-order low-pass filter using just a resistor ($R = 10.0$ k Ω) and a capacitor ($C = 0.653$ μ F). Calculate the cutoff frequency (in Hz) of her filter.
- Calculate the gain (G) of this filter at the noise frequency (3600 Hz). Is the noise amplitude attenuated enough to completely remove the noise?


Solution:

$$(a) \text{ A/D Quantizing (quantization) error} = \pm \frac{V_{\max} - V_{\min}}{2^{N+1}} = \pm \frac{10 - (-10) \text{ V}}{2^{12+1}} = \pm 0.0024414 \text{ V}$$

• So, the required gain of the filter is $G = \frac{|V_{\text{out}}|}{|V_{\text{in}}|}$ ← Set to quantizing error
 ← Set to input amplitude (of the noise)

• Recall, we want to attenuate the noise so much that it gets "lost" in the resolution or quantizing error of the A/D.

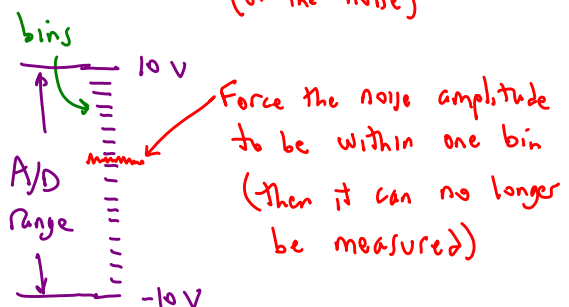[In other words, we set G small enough that the noise fits inside one bin of the A/D converter!]



$$G = \frac{|\pm 0.0024414 \text{ V}|}{|\pm 0.3 \text{ V}|} = 0.008138 = G_{\text{required}}$$


$$(b) f_{\text{cutoff}} = \frac{1}{2\pi RC} = \frac{1}{2\pi(10,000 \Omega)(0.653 \times 10^{-6} \text{ F})} \left(\frac{\text{F} \cdot \text{V}}{\text{C}} \right) \left(\frac{\text{C}}{\text{F} \cdot \text{A}} \right) \left(\frac{\text{A} \cdot \text{V}}{\text{V}} \right) = 24.3729 \text{ Hz}$$

$$f_{\text{cutoff}} \text{ of her filter} = 24.4 \text{ Hz}$$

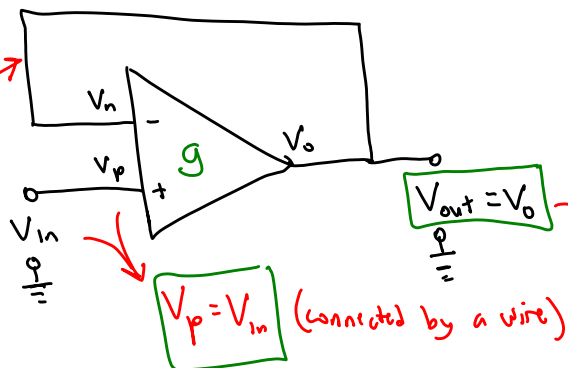(c) At $f = 3600 \text{ Hz}$ (noise), $G = \frac{1}{\sqrt{1 + \left(\frac{3600}{24.3729}\right)^2}} = 0.00677 = G_{\text{actual}}$

Thus, since $G_{\text{actual}} < G_{\text{required}}$, **THIS FILTER WILL DO THE JOB** Yes

DETAILED ANALYSIS OF A BUFFER (REAL OP-AMP)



• Eq. for the op-amp:

$$V_o = g(V_p - V_n) \quad \star (1)$$

Similarly, $V_{\text{out}} = V_o$ (connected by a wire)

• So, Eq. (1) becomes $V_o = V_{\text{out}} = g(V_{\text{in}} - V_n)$

But $V_n = V_o = V_{\text{out}}$, since these are all connected by a wire!

• Thus,
$$V_{\text{out}} = g(V_{\text{in}} - V_{\text{out}}) \quad \left[\text{or } V_o = g(V_{\text{in}} - V_o) \right]$$

• Do some algebra $\rightarrow V_{\text{out}}(1+g) = V_{\text{in}} \rightarrow V_{\text{out}} = \frac{g}{1+g} V_{\text{in}} \quad \star$

Exact equation for a buffer (op-amp has internal gain g)

Example numbers: For $V_{\text{in}} = \text{exactly } 5 \text{ V}$ & $g = 1 \times 10^6$ (typical g)
 then $V_{\text{out}} = \frac{1 \times 10^6}{1 + 1 \times 10^6} (5 \text{ V}) = 4.999995 \text{ V}$

This is so close to 5 that any voltmeter would read 5.0000 V

CONCLUSION: For a buffer, $V_{\text{out}} \approx V_{\text{in}}$ and $V_n \approx V_p$ (the error is negligible)

But, the exact relationship is
$$V_{\text{out}} = \frac{g}{1+g} V_{\text{in}}$$

Example: Op-amps


Given: The circuit shown, with

- $R_1 = 20 \text{ k}\Omega$
- $R_2 = 80 \text{ k}\Omega$

The supply voltages to the op-amp are +15 V and -15 V (not shown).

To do:

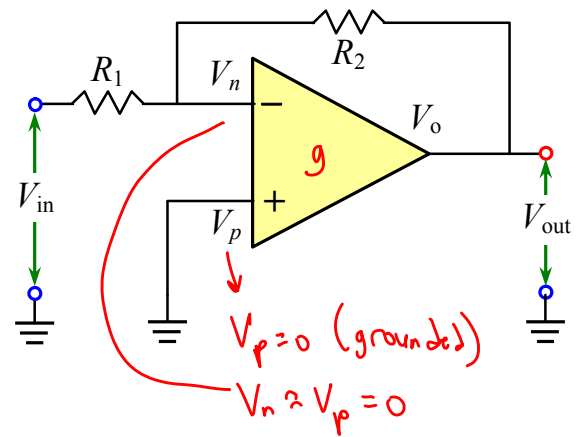(a) If the input voltage is $V_{in} = 1.50 \text{ V DC}$ and the op-amp is *ideal*, calculate the value of voltage V_n .



Solution:

- $V_p = 0$ since it is grounded
- For an ideal op-amp, $V_n = V_p$, so $V_n = 0$
- For a real op-amp, $V_n \approx V_p \approx 0$ because g is not ∞ (g typically $\sim 10^6$)
[V_n will be a very small voltage — millivolts or microvolts, depending on g]

(b) If the input voltage is $V_{in} = 2.50 \text{ V DC}$ and the op-amp is *real* (a type 741), calculate V_{out} (to 3 significant digits). [Note: You may still make the approximation $V_n \approx V_p$.]

Solution:

• This is an Inverting amplifier

(I remember it because the input goes into V_n not into V_p — a non-inverting amp is the opposite)

$$G = -\frac{R_2}{R_1} = -\frac{80}{20} = -4$$

Answer: $V_{out} \approx 10 \text{ V}$

(actually a little smaller since $g \neq \infty$, but the error is negligible)

$$V_{out} = G V_{in} = (-4)(2.50 \text{ V}) = -10.0 \text{ V (DC)}$$

(c) If the input voltage is $V_{in} = 4.50 \text{ V DC}$ and the op-amp is *real* (a type 741), calculate V_{out} (to 2 significant digits). [Note: You may still make the approximation $V_n \approx V_p$.]

Solution:

$$\text{• Here, } G = -4 \text{ still, so } V_{out} = -4(4.50 \text{ V}) = \underline{-18.0 \text{ V}}$$

• But, the op-amp cannot put out this large of a negative voltage
since $V_{supply}^- = -15 \text{ V}$ [The op-amp will saturate.]

• Actual $V_{out} \approx -14 \text{ V}$ (about a volt different than V_{supply}^-)