

Today, we will:

- Do some more example problems – op-amps
- Continue reviewing the pdf module: **op-amps (active filters, clipping circuits)**
- Discuss input and output impedance in more detail

Example: Op-amp circuits**Given:** The circuit shown, with

- $R_1 = 20 \text{ k}\Omega$
- $R_2 = 80 \text{ k}\Omega$

The supply voltages to the op-amp are +15 V and -15 V (not shown).

To do:(a) Is this an *inverting* or a *noninverting* amplifier?(b) For an *ideal* op-amp, when $V_{in} = 1.50 \text{ V DC}$, calculate V_n in Volts.

$$V_n \approx V_p = V_{in} \rightarrow \boxed{V_n = 1.50 \text{ V DC}}$$

(c) For an *ideal* op-amp, calculate the gain G of the circuit.

$$\text{For noninverting amplifier, } G = 1 + \frac{R_2}{R_1} = 1 + \frac{80 \text{ k}\Omega}{20 \text{ k}\Omega} = \boxed{5}$$

(Note: $G \neq R_2/R_1 = 4$)
Here, $G = 1 + R_2/R_1 = 5$

(d) For a *real* op-amp, when $V_{in} = 1.50 \text{ V DC}$, calculate V_{out} in Volts.

$$V_{out} = G V_{in} \approx 5 (1.50 \text{ V}) = \boxed{7.50 \text{ V}}$$

[actual voltage will differ, but by negligible microvolts, since $g \neq \infty$]

(e) For a *real* op-amp, when $V_{in} = 4.20 \text{ V DC}$, calculate V_{out} in Volts.

$$V_{out} = G V_{in} \approx 5 (4.20 \text{ V}) = 21.0 \text{ V} \times$$

No — op-amp cannot output more voltage than the supply voltage!

[The op-amp will saturate] →

• So, since $V_{supply}^+ = 15.0 \text{ V}$, we expect $V_{out} \approx 1 \text{ V}$ lower

$$\boxed{V_{out} \approx 14 \text{ V}}$$


Additional: Calculate the current I (n mA) through resistor R_1 .

• See circuit diagram above, where we label current I and its direction

• Ohm's law: $\Delta V = IR \rightarrow I = \frac{\Delta V}{R_1} = \frac{1.50 \text{ V} - 0 \text{ V}}{20,000 \Omega} \left(\frac{\text{A} \cdot \Omega}{\text{V}} \right) \left(\frac{1000 \text{ mA}}{\text{A}} \right) = 0.075 \text{ mA}$

Answer → $\boxed{I = 0.075 \text{ mA}}$
 $\boxed{(75 \mu\text{A})}$

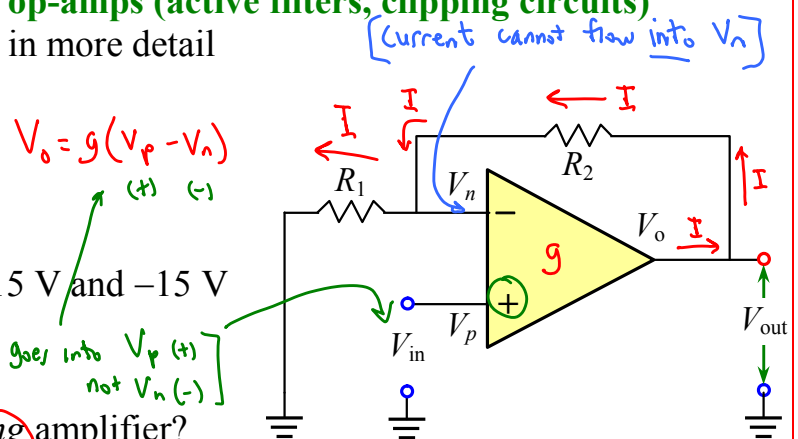→ This is very small because R_1 is so big
[One reason why we use large R 's in these circuits]




Example: Op-amp circuits

Given: Two voltage input signals, V_1 and V_2 are to be combined to produce an output voltage: $V_o = 4(3V_1 + V_2)$.

To do: Design a circuit that will produce this output, using only op-amps and resistors. Use *inverting* amplifiers [which deal with noise better than noninverting amplifiers], as will be discussed later. Assume that the only resistors you have are 20 k Ω .


Solution: • Our goal is $V_o = 4(3V_1 + V_2)$ There are many options

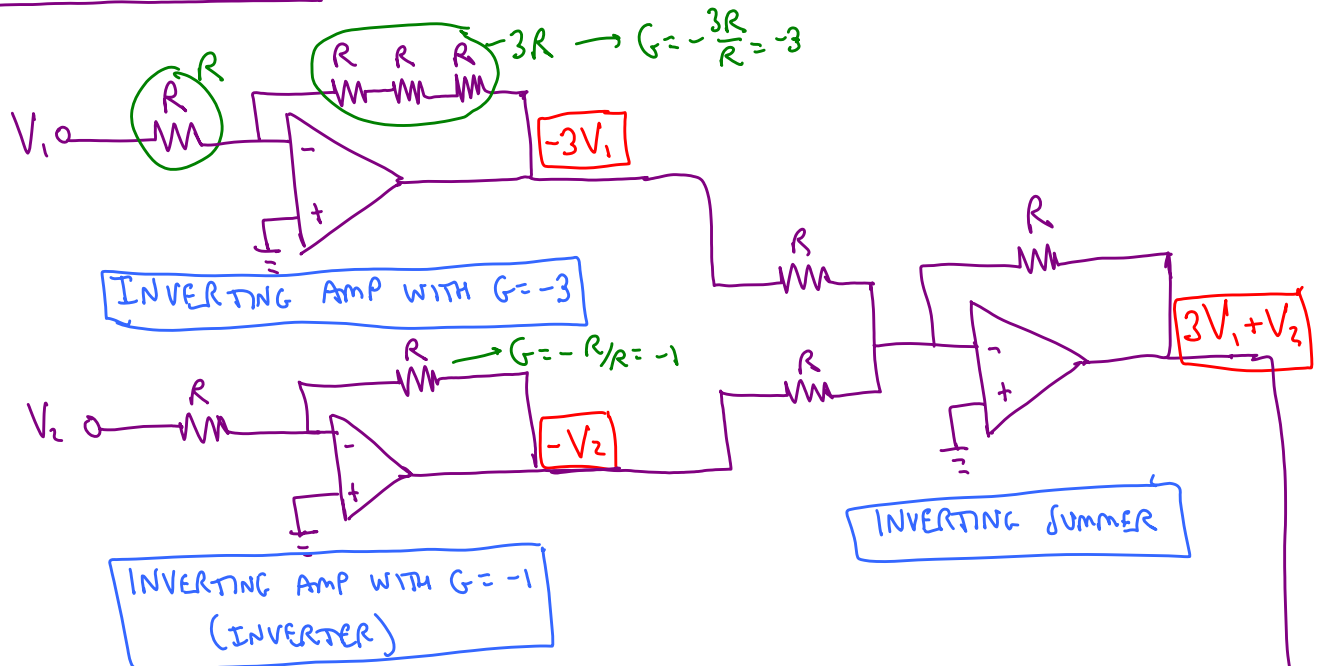• Brute Force Method (one step at a time):




• We multiplied V_1 by -3 , multiplied V_2 by -1 , added (and inverted) them.

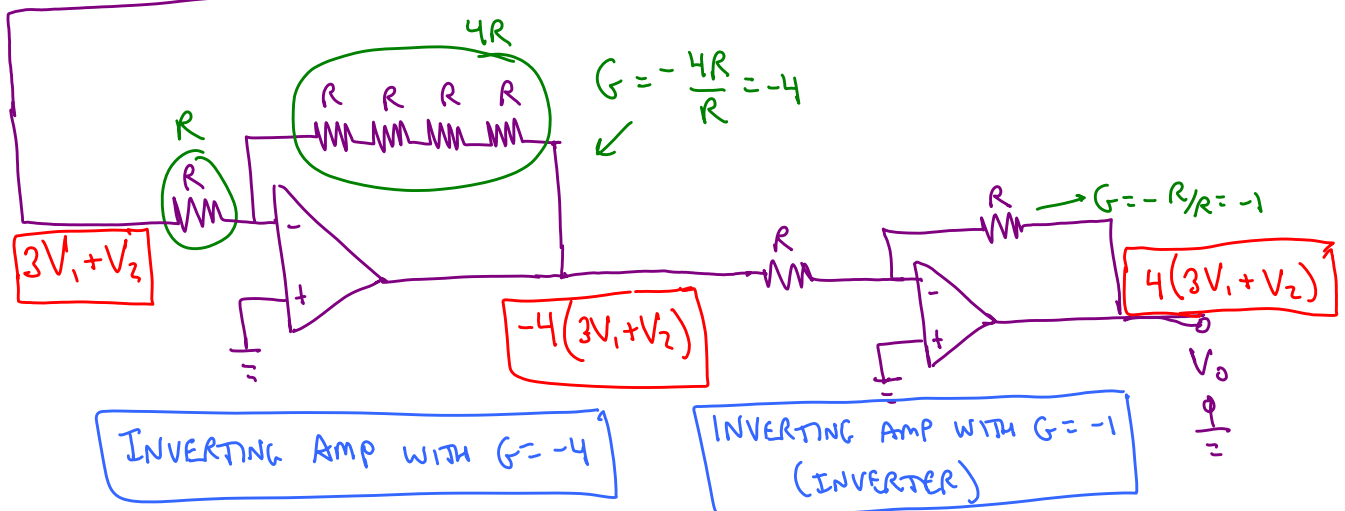• Now we still need to multiply the sum by 4:




• Finally, invert to get the desired result

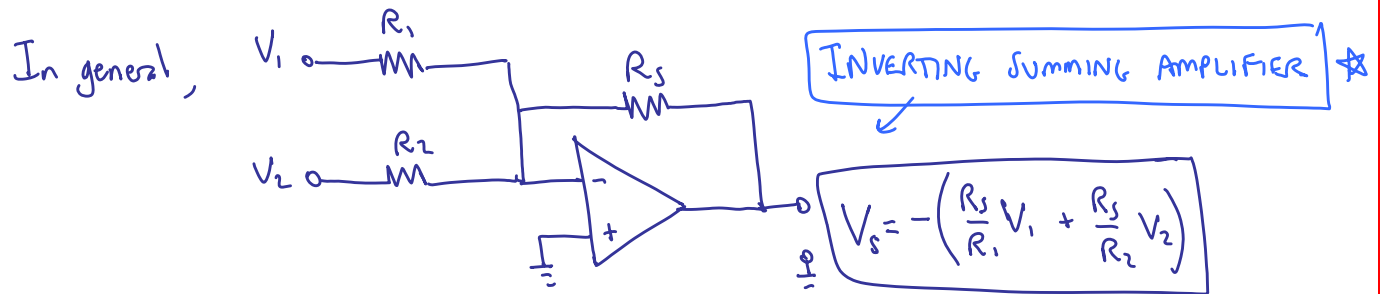- The above (brute force) circuit requires 5 op-amps and 16 resistors
- We can do much better (less complicated circuit with fewer components)
- E.g., combine the amplification and the summing



Here, we choose $\frac{R_s}{R_1} = 12$ so that V_1 gets multiplied by 12
 $\therefore \frac{R_s}{R_2} = 4$ so that V_2 gets multiplied by 4
 because $V_o = 4(3V_1 + V_2) = 12V_1 + 4V_2$

Revised circuit:

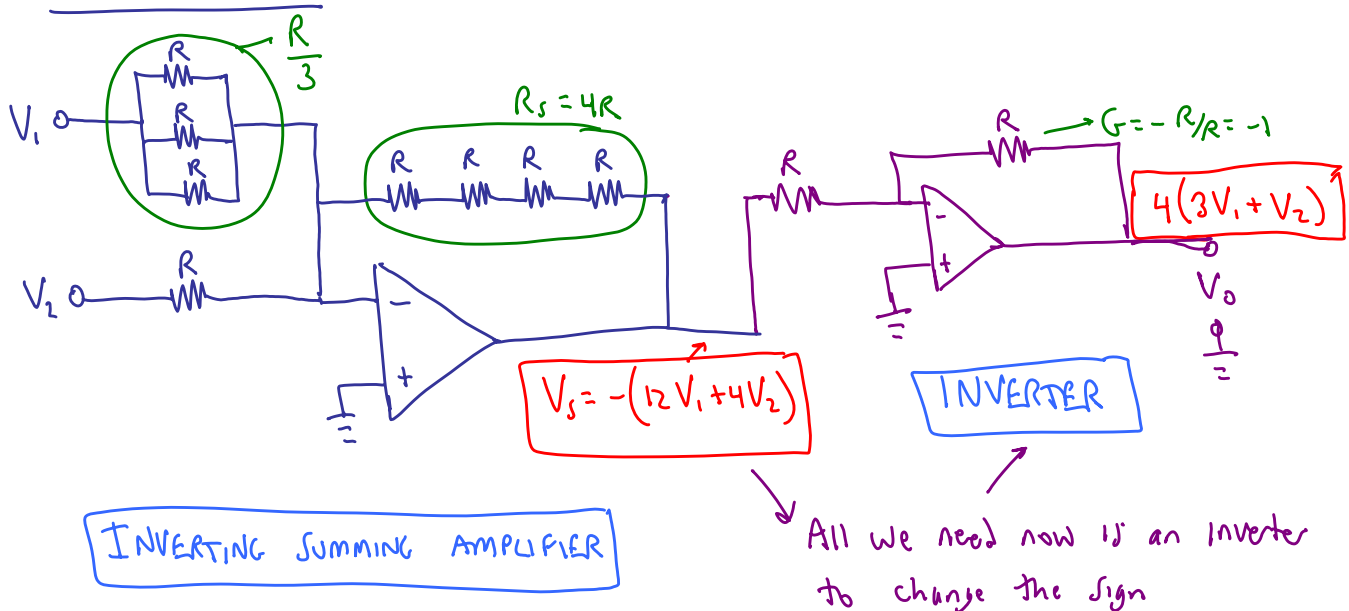

Now we are using only 2 op-amps and 10 resistors (much better than the brute force method)

Example: Op-amp circuits


Given: The circuit shown to the right.

(a) To do: Calculate V_o in terms of V_i .

Solution: This is an inverting amplifier

$$\text{With } G = -\frac{R_2}{R_1} = -\frac{20}{10} = -2$$

$$\text{So, } \boxed{V_o = -2V_i}$$

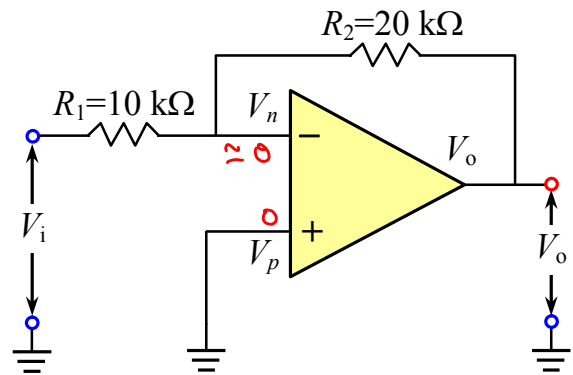


(b) To do: Calculate the input impedance of the amplifier.

Solution: ★ The input impedance of an inverting amplifier is $\approx R_1$ since $V_n \approx V_p = 0$


• Here, $\boxed{\text{Input impedance} \approx R_1 = 10 \text{ k}\Omega}$ [This is what V_i "sees" → 

(c) To do: Suppose V_i is supplied by a cheap power supply with an output impedance of 5.0Ω . The power supply is adjusted to provide exactly 10 V ($V_s = 10 \text{ V}$). Thus, $V_i = 10 \text{ V}$ when there is *no load* on the supply. Calculate the voltage V_i when this power supply is connected to the above op-amp circuit (i.e., we add a *load* to the power supply).

Solution:

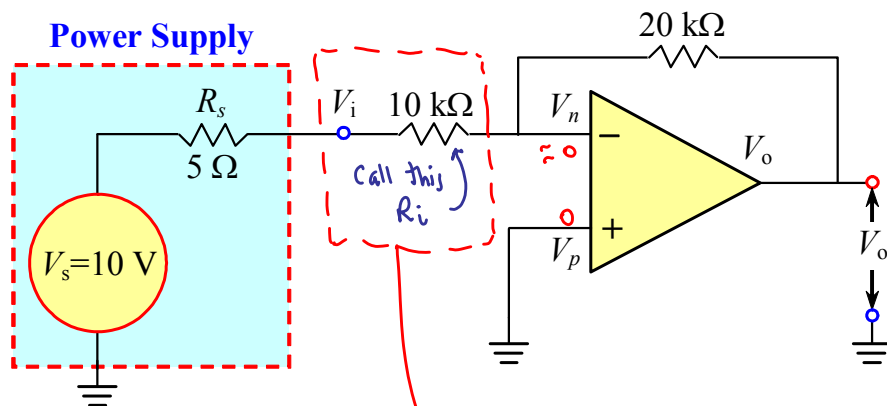


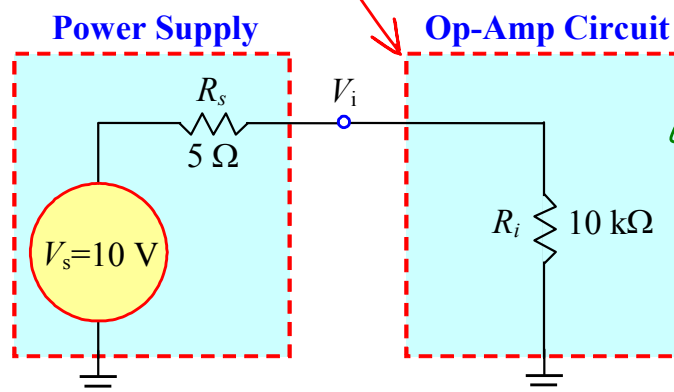Since the input impedance of an inverting amplifier op-amp circuit is equal to R_1 , the input impedance here is $10 \text{ k}\Omega$. Thus, the equivalent circuit (from the power supply's point of view) is:



[The input impedance acts like a resistor in series with the output impedance resistor of the power supply.]

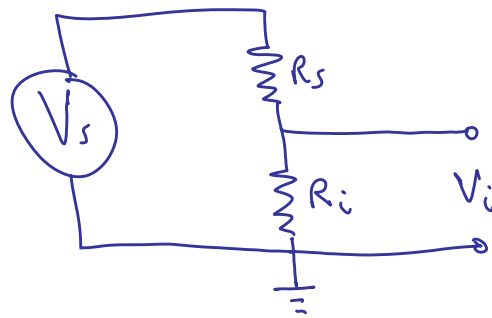Circuit analysis — this is just a voltage divider circuit!



$$V_i = \frac{R_i}{R_i + R_s} V_s$$

Numbers: For $V_s = 10 \text{ V}$; $R_i = R_i = 10 \text{ k}\Omega$; $R_s = 5 \Omega$

$$V_i = \frac{10,000 \Omega}{10,000 + 5 \Omega} (10 \text{ V}) = 9.995 \text{ V} \rightarrow V_i = 9.995 \text{ V}$$

Notice that $V_i < V_s$ ($V_i < 10 \text{ V}$) → We have reduced the power supply's voltage by adding another circuit downstream

This voltage drop is called input loading ☆

[We are changing the very voltage we are trying to amplify]

Conclusion & Summary

Good electronics devices should have:

- ☆ Very high input impedance → low input loading
- ☆ Very low output impedance → low output loading

☆ This is why good voltmeters, oscilloscopes, A/D cards, etc. have input impedances on the order of tens or hundreds of megaohms


E.g. If measuring the 10 V power supply with a voltmeter with $R_i = 6.0 \text{ M}\Omega$

$$V_{\text{measured}} = \frac{6.0 \times 10^6 \Omega}{6.0 \times 10^6 \Omega + 5 \Omega} (10 \text{ V}) = \underline{9.999992 \text{ V} \approx 10.000 \text{ V}}$$

Negligible input loading ☆

• On the other hand, low input impedance leads to significant input loading.

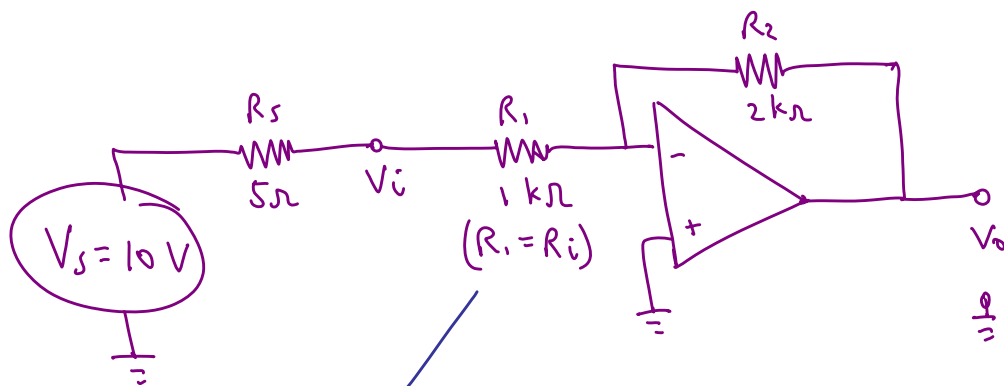• E.g., Suppose we use $R_1 = 1 \text{ k}\Omega$ instead of $10 \text{ k}\Omega$
 $\therefore R_2 = 2 \text{ k}\Omega$ instead of $20 \text{ k}\Omega$



Now, the input impedance is only $1 \text{ k}\Omega$ instead of $10 \text{ k}\Omega$

$$V_i = \frac{R_i}{R_i + R_S} V_S = \frac{1000 \Omega}{1000 + 5 \Omega} (10 \text{ V}) = \boxed{9.95 \text{ V} = V_i}$$

This is really noticeable input loading

• Also, compare the power dissipated through R_1 for $R_1 = 1 \text{ k}\Omega$ & $10 \text{ k}\Omega$

$$R = 1 \text{ k}\Omega: \dot{W} = VI = \frac{V^2}{R} = \frac{(9.95 \text{ V})^2}{1000 \Omega} \left(\frac{\text{W} \cdot \Omega}{\text{V}^2} \right) = 0.099 \text{ W} \approx \underline{\underline{0.10 \text{ W}}}$$

$$R = 10 \text{ k}\Omega: \dot{W} = \frac{(9.95 \text{ V})^2}{10,000 \Omega} \left(\frac{\text{W} \cdot \Omega}{\text{V}^2} \right) = 0.0099 \text{ W} \approx \underline{\underline{0.01 \text{ W}}}$$

(ten times smaller power)

★ This is another reason why we like to use large resistors in op-amp circuits (waste less power)

Typical → $10 \text{ k}\Omega < R < 100 \text{ k}\Omega$
 (goal) ★

Extreme cases:
 $1 \text{ k}\Omega < R < 1 \text{ M}\Omega$