


Today, we will:

(Gain Bandwidth Product)

- Do another example problem – op-amps with GBP effects.
- Begin the pdf module: **Stress, Strain, and Strain Gages**, and do some examples.

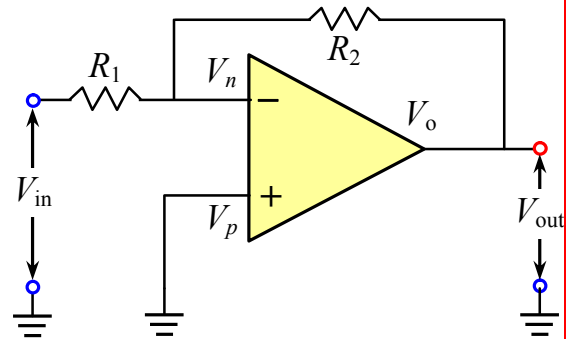Example: Op-amp circuit with GBP effects

Given: Ben amplifies the voltage output of a microphone by a factor of 1000 using an inverting amplifier as sketched, with $R_1 = 1.00 \text{ k}\Omega$ and $R_2 = 1.00 \text{ M}\Omega$. The quality of the amplified music sounds odd to Ben, particularly at high frequencies, but he is clueless as to why this is happening. His friend Ashley took M E 345 and remembers something about GBP effects with op-amps. She looks up the specs for Ben's op-amp: $\text{GBP}_{\text{noninverting}} = 0.450 \text{ MHz}$. She explains to Ben that his op-amp is acting like a first-order low-pass filter, and that is why he is losing some of the high frequencies in his music.



$$G_{\text{theory}} = -\frac{R_2}{R_1} = \frac{-1000 \text{ k}\Omega}{1.00 \text{ k}\Omega} = -1000 \checkmark$$

To do:

- Calculate the internal cutoff frequency of this op-amp circuit.
- Compare the *theoretical* gain and the *actual* gain of this circuit at $f = 10,000 \text{ Hz}$.

Solution: For an inverting op-amp amplifier, we need to convert the GBP manufacturer's

(a) [spec from noninverting (the spec for GBP is given for noninverting amplifiers)]

• From the learning module,

$$\text{GBP}_{\text{inverting}} = -\frac{R_2}{R_1 + R_2} \text{GBP}_{\text{noninverting}}$$

(notice that $\text{GBP}_{\text{inverting}}$ is negative) $\downarrow$

$$= -\frac{1000 \text{ k}\Omega}{(1+1000) \text{ k}\Omega} (0.450 \text{ MHz}) = \underline{-0.44955 \text{ MHz}}$$

• The rest of the algebra is pretty much the same as for noninverting amplifiers:

$$f_c = \frac{\text{GBP}_{\text{inverting}}}{G_{\text{theory}}} = \frac{-0.44955 \text{ MHz}}{-1000} = \boxed{449.55 \text{ Hz} = f_c}$$

[This circuit acts like a low-pass filter with $f_{\text{cutoff}} = 449.55 \text{ Hz}$!]

This is the "GBP effect"

(G_{theory}) $\downarrow$

$$(b) \text{ At } f = 10,000 \text{ Hz}, G_{\text{actual}} = G_{\text{theory}} G_{\text{GBP, inverting}} = \left(-\frac{R_2}{R_1}\right) \frac{1}{\sqrt{1 + (f/f_c)^2}}$$



numbers: $G_{\text{theory}} = -1000$ but $G_{\text{actual}} = -1000 \frac{1}{\sqrt{1 + (10,000/449.55)^2}} = \boxed{-44.9 = G_{\text{actual}}}$

★ Ben should use a 2-stage amplifier !

Smaller by a factor > 20 !

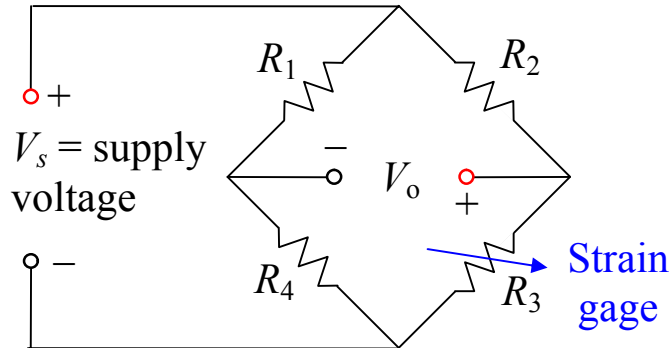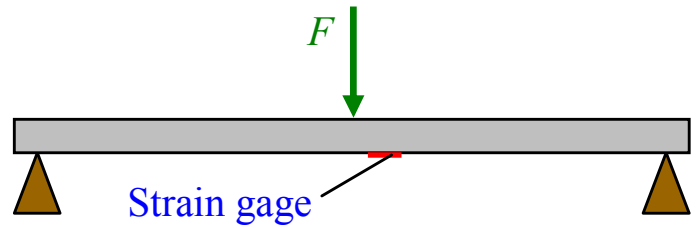
Example: Strain gages

Given: We are measuring the strain on the surface of a beam. The beam's modulus of elasticity is $E = 193 \text{ GPa}$. We use one strain gage on the bottom of the beam, as shown; the strain gage factor is $S = 2.02$. We construct a quarter bridge Wheatstone bridge circuit, with the strain gage on resistor 3, as sketched below. All resistors, including the strain gage itself (when unloaded) are 120Ω . The supply voltage is 5.00 V DC , and the bridge is initially balanced when there is no load.



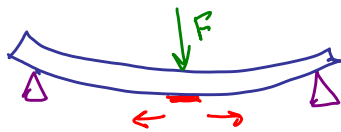(a) To do: Will V_o be positive or negative when a downward load is added?

Solution: When we push down, the strain gage will stretch (positive strain)



(R increases when the strain gage is in tension)

(The strain gage is in tension.)

Therefore, δR_3 is positive when we apply the force.

$\oplus$ for $\oplus F$

Recall from the pdf notes:

$$\frac{V_o}{V_s} \approx \frac{R_{2,\text{initial}} R_{3,\text{initial}}}{(R_{2,\text{initial}} + R_{3,\text{initial}})^2} \left(\frac{\delta R_1}{R_{1,\text{initial}}} - \frac{\delta R_2}{R_{2,\text{initial}}} + \frac{\delta R_3}{R_{3,\text{initial}}} - \frac{\delta R_4}{R_{4,\text{initial}}} \right)$$

$\delta R_1, \delta R_2, \delta R_4$ all = 0 since these are just fixed resistors in the bridge.

δR_3 is the only non-zero change in resistance, and it is $\oplus$ when F is $\oplus$

$$\therefore V_o \approx V_s \frac{R_{2,\text{initial}} R_{3,\text{initial}}}{(R_{2,\text{initial}} + R_{3,\text{initial}})^2} \frac{\delta R_3}{R_{3,\text{initial}}} \quad (1)$$

Answer:

V_o is positive when F is positive downward
(Always wise to have V_o increase i. $\oplus$ ve when F is increasing i. $\oplus$ ve)

(b) To do: For a loading in which $V_0 = 1.25$ mV, calculate the strain ϵ_a in units of microstrain.

Solution: LONG WAY:

• For $V_0 = 1.25$ mV, we use the equation for strain vs resistance:

$$\frac{\delta R}{R} = S \epsilon_a \rightarrow \epsilon_a = \frac{\delta R}{R S} = \frac{\delta R_3}{R_{3, \text{initial}} \cdot S}$$

• But, using Eq. (1) of Part (a), we know that

$$\frac{\delta R_3}{R_{3, \text{initial}}} = \frac{V_0}{V_s} \frac{(R_{2, \text{initial}} + R_{3, \text{initial}})^2}{R_{2, \text{initial}} \cdot R_{3, \text{initial}}}$$

Plug this into here

• Algebra ...

$$\epsilon_a = \frac{1}{S} \frac{V_0}{V_s} \left[\frac{(R_{2, \text{initial}} + R_{3, \text{initial}})^2}{R_{2, \text{initial}} \cdot R_{3, \text{initial}}} \right]$$

Note that if $R_{2, \text{initial}} = R_{3, \text{initial}}$, $[] = 4$

Numbers

$$\epsilon_a = \frac{1}{2.02} \frac{1.25 \times 10^{-3} \text{ V}}{5.00 \text{ V}} \left[\frac{(120 \Omega + 120 \Omega)^2}{120 \Omega \cdot 120 \Omega} \right] = \underline{4.950 \times 10^{-4}}$$

• In units of microstrain, $\epsilon_a = 4.950 \times 10^{-4} \left(\frac{10^6 \mu\text{strain}}{1} \right) = 495. \mu\text{strain}$

Answer: $\epsilon_a = 495. \mu\text{strain}$

unity conversion factor (to 3 digits)

SHORT WAY:

OR, Use our approximate eq. for a quarter bridge Wheatstone bridge:

$$\epsilon_a = 4 \frac{V_0}{V_s} \frac{1}{S} = 4 \frac{1.25 \times 10^{-3} \text{ V}}{5.00 \text{ V}} \frac{1}{2.02} \left(\frac{10^6 \mu\text{strain}}{1} \right) = \boxed{495. \mu\text{strain}}$$

(c) **To do:** If the material is cold work tool steel with modulus of elasticity $E = 193 \text{ GPa}$ (at room temperature), calculate the axial stress (in MPa) in the beam under this load.

Solution:

$$\sigma_a = E \cdot \epsilon_a$$

axial stress ← σ_a
Young's modulus ← E
axial strain ← ϵ_a

(Be careful - power of 10 errors)



$$\begin{bmatrix} \text{mega} = 10^6 \\ \text{micro} = 10^{-6} \\ \text{giga} = 10^9 \end{bmatrix}$$

from Part (b)

$$\text{Here, } \sigma_a = (193 \times 10^9 \frac{\text{N}}{\text{m}^2}) (4.950 \times 10^{-4}) \left(\frac{1 \text{ Pa}}{\text{N/m}^2} \right) \left(\frac{1 \text{ MPa}}{10^6 \text{ Pa}} \right) = 95.5 \text{ MPa} = \sigma_a$$

(d) **To do:** Suppose we want more sensitivity, so we glue another strain gage on *top* of the beam. Which resistor should we use for this second active strain gage?

Solution:

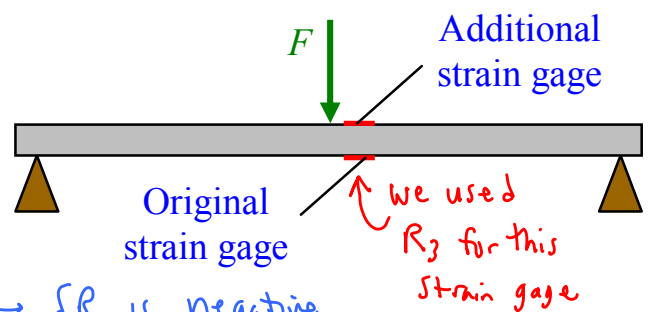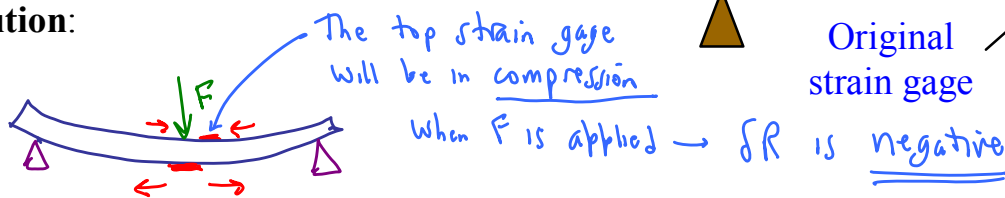

So, we pick one of the R 's in the bridge that has a negative sign:

Again from the pdf notes:

$$\frac{V_o}{V_s} \approx \frac{R_{2,\text{initial}} R_{3,\text{initial}}}{(R_{2,\text{initial}} + R_{3,\text{initial}})^2} \left(\frac{\delta R_1}{R_{1,\text{initial}}} - \frac{\delta R_2}{R_{2,\text{initial}}} + \frac{\delta R_3}{R_{3,\text{initial}}} - \frac{\delta R_4}{R_{4,\text{initial}}} \right)$$

(+) (-) (+) (-)

Answer: Pick either R_2 or R_4 so that $V_o = -(-\delta R) = (+)$ when F is applied

(e) **To do:** For the setup of Part (d) with the same strain as in Part (b), calculate output voltage V_o .

Solution: - We have doubled the sensitivity of the circuit $\rightarrow$ it is now a half-bridge circuit. $n=2$ for a half bridge

So, the voltage also doubles: $V_o = V_s \epsilon_a \frac{n}{4} S = (5.00 \text{ V}) (4.95 \times 10^{-4}) \frac{2}{4} (2.02) = 2.50 \text{ mV}$