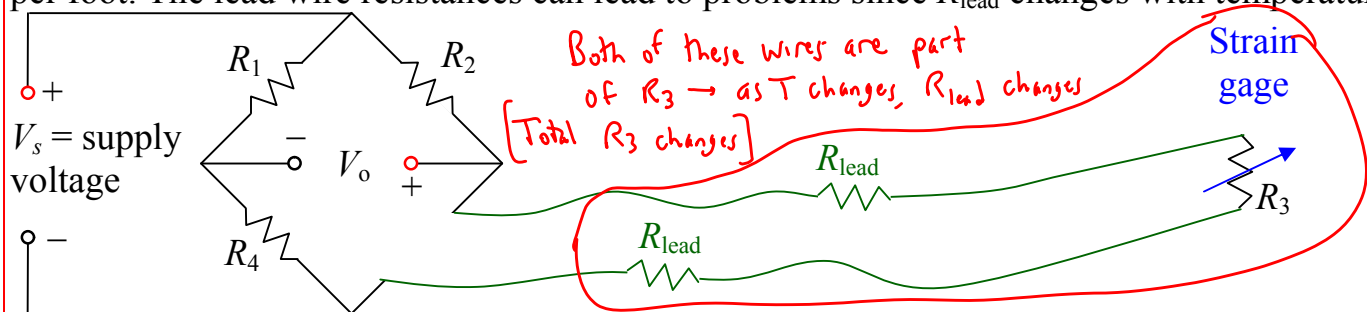


Today, we will:

- Discuss how to compensate for strain gages with long lead wires
- Do a **review** example problem – A/D converters, op-amps, filters, and strain gages


Example: Strain gage with long lead wires – how to compensate

Given: A quarter-bridge strain gage circuit is constructed with $120\text{-}\Omega$ resistors and a $120\text{-}\Omega$ strain gage as usual. The main problem here is that the experiment is very far away – the lead wires going to the strain gage are 40 ft long, and the lead wires have a resistance of $0.026\text{ }\Omega$ per foot. The lead wire resistances can lead to problems since R_{lead} changes with temperature.



To do: Devise a modified circuit that will cancel out the effect of the lead wires.

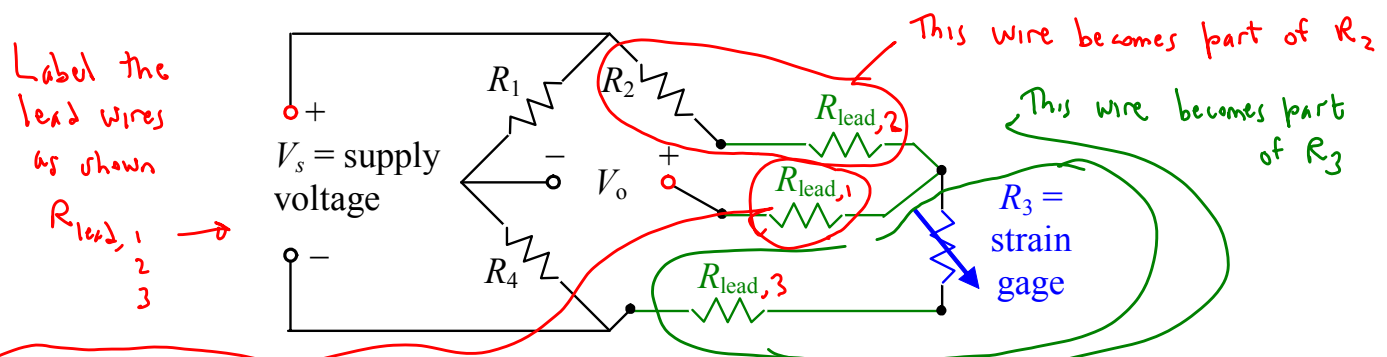Solution: A clever “trick”, using 3 wires connected to the strain gage rather than just 2:




Recall the approximate equation for V_o when all four resistors of the Wheatstone bridge have small changes in resistance:

$$\frac{V_o}{V_s} \approx \frac{R_{2,\text{initial}} R_{3,\text{initial}}}{(R_{2,\text{initial}} + R_{3,\text{initial}})^2} \left(\frac{\delta R_1}{R_{1,\text{initial}}} - \frac{\delta R_2}{R_{2,\text{initial}}} + \frac{\delta R_3}{R_{3,\text{initial}}} - \frac{\delta R_4}{R_{4,\text{initial}}} \right)$$

$\delta R_{\text{lead},2} = \delta R_{\text{lead},3}$
Since the wires are exposed to the same temperature variations

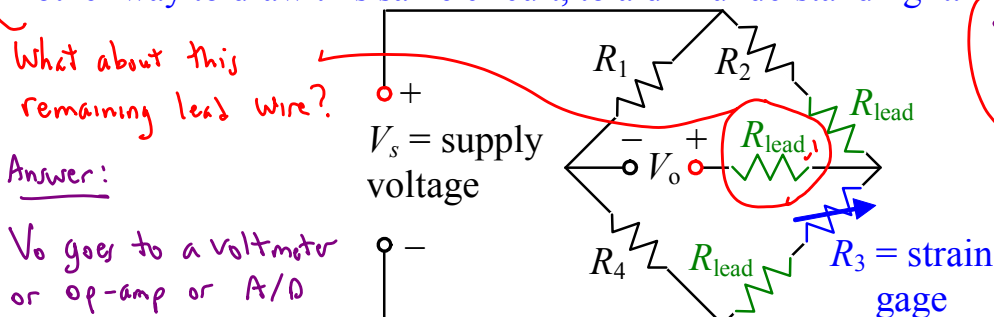Another way to draw this same circuit, to aid in understanding it:



Answer:

V_o goes to a voltmeter or op-amp or A/D or something with a

very high input impedance $\rightarrow$ So, negligible current flows through $R_{\text{lead},1}$ $\therefore$ negligible ΔV

So – the lead wire resistances cancel each other out!

clever!

V_o is unaffected by changes in $R_{\text{lead},1}$

Example: Strain gages and digital data acquisition [a comprehensive review problem]

Given: A quarter-bridge Wheatstone bridge circuit is used with a strain gage to measure strains up to $\pm 1000 \mu\text{strain}$ for a beam vibrating at a maximum frequency of 50 Hz.

- the supply voltage to the Wheatstone bridge is $V_s = 5.00 \text{ V DC}$
- all Wheatstone bridge resistors and the strain gage itself are 120Ω
- the circuit is initially balanced at zero strain
- the strain gage factor for the strain gage is $S = 2.04$
- there is some unwanted noise in output V_o : $f_{\text{noise}} = 3600 \text{ Hz}$ and amplitude $= \pm 0.50 \text{ mV}$
- the output voltage V_o is sent into a 12-bit A/D converter with a range of $\pm 5 \text{ V}$
- op-amps, resistors, and capacitors are available in the lab
- all op-amps have a GBP (noninverting) of 1.2 MHz

To do: Design a circuit with the highest possible resolution (i.e., a circuit that utilizes the full range of the A/D converter), and minimizes the noise.

Solution:


First, we calculate $V_{o,\text{max}} = \text{max voltage output from the strain gage circuit:}$

$$V_{o,\text{max}} = V_s \epsilon_a \frac{n}{4} S = (5.00 \text{ V}) (1000 \times 10^{-6}) \frac{1}{4} (2.04) = 2.55 \times 10^{-3} \text{ V} = \text{maximum}$$

Thus, V_o varies between -2.55 mV and $+2.55 \text{ mV}$. Now, to utilize the full range of the A/D converter, we need to amplify by a factor of $\leftarrow \text{Too small!}$

$$G = \frac{\pm 5.00 \text{ V}}{\pm 2.55 \times 10^{-3} \text{ V}} = \pm 1960.78 \text{ [sign depends on type of amplifier]}$$

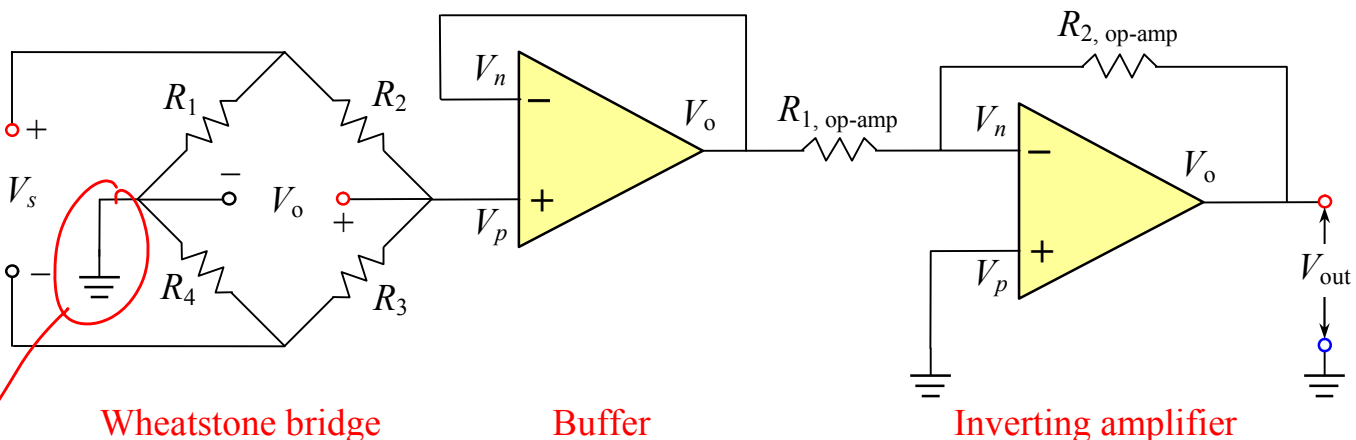We suggest this circuit (single stage inverting amplifier) as a starting point:



To achieve the required gain, we would use, say, $R_{1, \text{op-amp}} = 1 \text{ k}\Omega$, and $R_{2, \text{op-amp}} = 1.96 \text{ M}\Omega$.

Questions:

1. Why do we ground the Wheatstone bridge at V_o^- instead of at the bottom of the bridge?

• Have to ground somewhere

• Forcing $V_o^- = 0$ guarantees that V_o^+ will range from -2.55 to $+2.55 \text{ mV}$ relative to ground

2. Why did we put a buffer between the Wheatstone bridge and the amplifier?

• The bridge circuit is sensitive to downstream circuits $\rightarrow V_o$ can change if current is drawn

• So $\rightarrow$ Add a buffer to provide a very high input impedance [Nothing downstream of the buffer will affect V_o]

3. Why are we using an *inverting* (rather than a noninverting) amplifier?

(CMRR noise)

Recall — Inverting amps are better at reducing noise if we care about noise here.


4. To get positive V_{out} when the strain is positive, which resistor should be the strain gage?

Since we are inverting, use one of the $\ominus$ ve resistors — R_2 or R_4

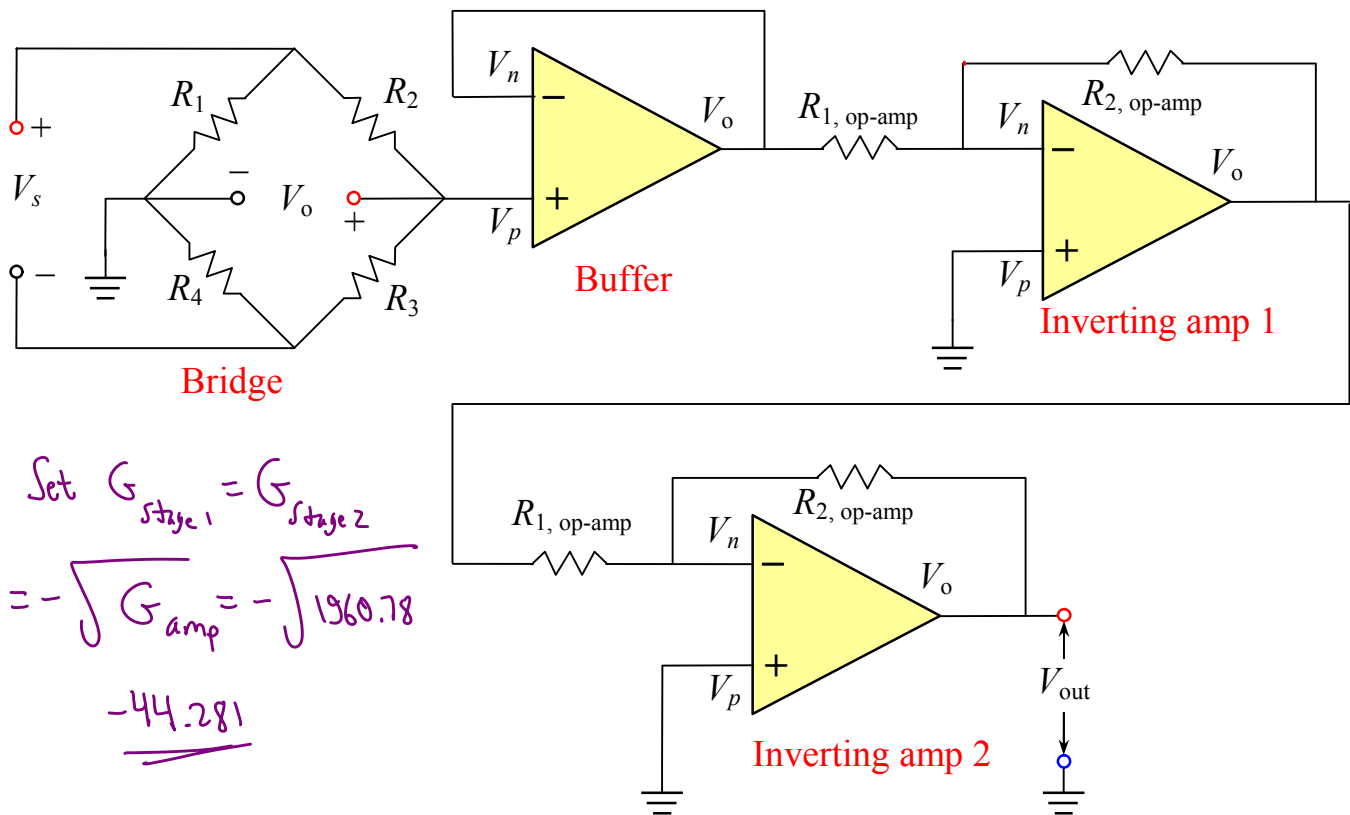5. Why is this circuit not so great, and what should we do to improve it?

Answers:

- $R_{1, \text{op-amp}} = 1 \text{ k}\Omega$ is at the lower recommended limit (not so great input impedance)
- $R_{2, \text{op-amp}}$ exceeds the recommended $1 \text{ M}\Omega$ limit (leads to stray capacitance effects)
- G is huge, and can lead to GBP effects as discussed previously
- To improve this circuit, let's instead construct a **two-stage amplifier**:



Set $G_{\text{stage 1}} = G_{\text{stage 2}}$
 $= -\sqrt{G_{\text{amp}}} = -\sqrt{1960.78}$
 -44.281

In this case, we can choose better values of the op-amp resistors. Namely, the gain of each amplifier is the square root of the total gain, i.e.,

$$G_{\text{stage}} = -\sqrt{1960.78} = -44.281$$

so we choose, for example, $R_{1, \text{op-amp}} = 10.0 \text{ k}\Omega$, and $R_{2, \text{op-amp}} = 442.8 \text{ k}\Omega$.

Much better since
 $R_1 > 1 \text{ k}\Omega$
 $R_2 < 1 \text{ M}\Omega$

Questions:

1. To get positive V_{out} when the strain is positive, which resistor should be the strain gage?


Now we are inverting twice $(\ominus\ominus = \oplus) \rightarrow$ So use R_1 or R_3 as the strain gage *

2. What should we add to get rid of the high frequency (3600 Hz) noise?


Recall, $f_{\text{signal}} \approx 50 \text{ Hz}$
 $f_{\text{noise}} \approx 3600 \text{ Hz}$

Use a low-pass filter to attenuate the high frequency noise

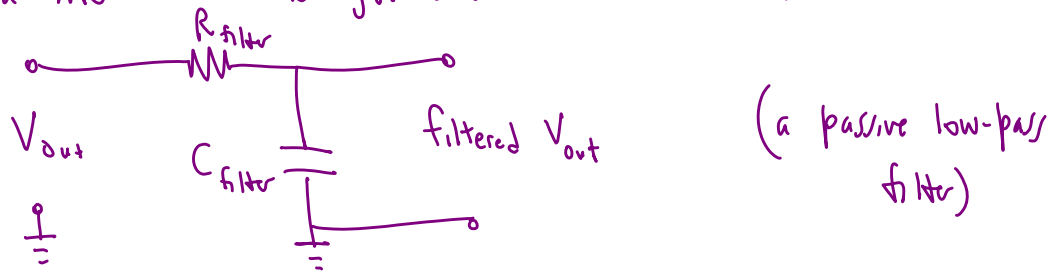- How to add a filter → could just add it at the end:



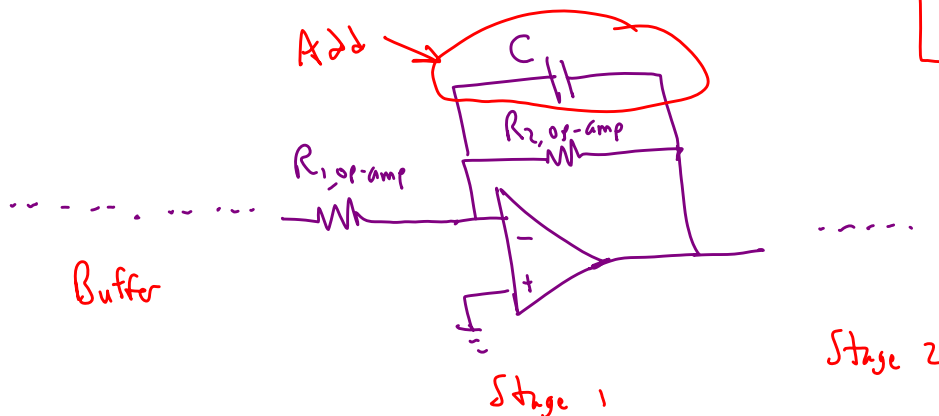- OR- better, since we already have an inverting amplifier, add a capacitor to convert the inverting amplifier into an active low-pass filter: Inverting amplifier



What C to use? → Since $f_{\text{signal}} = 50 \text{ Hz}$, let's pick $f_{\text{cutoff}} = 150 \text{ Hz}$
 So that we do not attenuate the desired frequency content.

Recall, $f_{\text{cutoff}} = \frac{1}{2\pi R_{2,\text{op-amp}} C} \rightarrow C = \frac{1}{2\pi R_{2,\text{op-amp}} f_{\text{cutoff}}}$

Recall,
 R_2 is the one
 that forms f_{cutoff}
 for an active low-pass filter

$$C = \frac{1}{2\pi (442800 \Omega) (150 \frac{1}{s})} \left(\frac{\Omega \cdot A}{V} \right) \left(\frac{C}{s \cdot A} \right) \left(\frac{F \cdot V}{C} \right)$$

$$C = 2.396 \times 10^{-9} \text{ F} \approx 2.40 \text{ pF} \quad (\text{picoFarad})$$

or $C \approx 0.00240 \mu\text{F}$

- For practice, calculate the GBP effects for our 2-stage amplifier ← Try this on your own
- Summary: $\left. \begin{array}{l} \text{GBP}_{\text{inverting}} = 1.173 \text{ MHz} \\ f_c = 26500 \text{ Hz} \end{array} \right\} \begin{array}{l} @ f = 50 \text{ Hz}, G_{\text{GBP}} = 0.999998 \text{ (negligible)} \\ @ f = 3600 \text{ Hz}, G_{\text{GBP}} = 0.99089 \text{ (also almost negligible effect)} \end{array}$

QUESTION: Does this filter "completely" remove the noise for our A/D?
I.e., have we reduced the noise amplitude below the resolution of the A/D?

SOLUTION: • Our A/D is ^{N=12} 12-bit with a range from $\overset{V_{min}}{\downarrow} \underline{-5}$ to $\overset{V_{max}}{\downarrow} \underline{5}$ V

• Quantization error = $\pm \frac{V_{max} - V_{min}}{2^{N+1}} = \frac{5 - (-5) \text{ V}}{2^{13}} = \underline{\pm 0.00122 \text{ V}}$
= $\underline{\pm 1.22 \text{ mV}}$

• Compare to the noise amplitude:

[Careful! We amplify twice, filter once, i. have GBP effects too]

$|V_{noise}|_{in} = \overset{\text{given}}{\pm 0.50 \text{ mV}}$

✓ [We don't care about the $\oplus$ or $\ominus$ signs here]

$$|V_{noise}|_{out} = |V_{noise}|_{in} \cdot |G_{amp1}| \cdot |G_{GBP,amp1}| \cdot |G_{filter}| \cdot |G_{amp2}| \cdot |G_{GBP,amp2}|$$

$$= (0.50 \text{ mV})(44.281)(0.99089) \left(\frac{1}{\sqrt{1 + \left(\frac{3600}{150}\right)^2}} \right) (44.281)(0.99089)$$

$$= \underline{40.07 \text{ mV}}$$

→ Since this is greater than the quantizing error, we have not removed the noise ★

• What to do? — Add another capacitor to the stage 2 amp to turn it also into an active low-pass filter / inverting amplifier ★

• Re-calculate (multiply the above by $\frac{1}{\sqrt{1 + \left(\frac{3600}{150}\right)^2}}$ again)

• Get $|V_{noise}|_{out} = \underline{1.67 \text{ mV}} \rightarrow \text{Still} > 1.22 \text{ mV} = \text{quantizing error, but not by much}$

[We almost remove the noise with two filters]

• EXTRA → Calculate the Signal-to-noise ratio (SNR) for the original input & for the output of our circuit (signal conditioned)

• Recall, $SNR = \left(\frac{\text{Ampl. signal}}{\text{Ampl. noise}} \right)^2$ by definition ; $SNR_{dB} = 20 \log_{10} \left(\frac{\text{Ampl. signal}}{\text{Ampl. noise}} \right)$

Here, Ampl. noise = $|V_{noise}|$, Ampl. signal = $|V_{signal}|$, etc.

• INPUT (original signal) : $\left. \begin{array}{l} |V_{signal}| = 2.55 \text{ mV} \\ |V_{noise}| = 0.50 \text{ mV} \end{array} \right\} \begin{array}{l} SNR_{in} = \left(\frac{2.55}{0.50} \right)^2 = 26.01 \\ SNR_{dB, in} = 20 \log_{10} \left(\frac{2.55}{0.50} \right) \end{array}$

Not very good → $SNR_{dB, in} = 14.2 \text{ dB}$

• OUTPUT (after signal conditioning)

$$|V_{signal}|_{out} = |V_{signal}|_{in} \cdot G_{amp}^2 \cdot G_{filter}^2 \cdot G_{GBP}^2$$

$$= (2.55 \text{ mV}) \cdot (44.281)^2 \left(\frac{1}{\sqrt{1 + \left(\frac{50}{150} \right)^2}} \right)^2 (0.999998)^2 = \underline{\underline{4500 \text{ mV}}}$$

$$|V_{noise}|_{out} = |V_{noise}|_{in} \cdot G_{amp}^2 \cdot G_{filter}^2 \cdot G_{GBP}^2$$

$$= (0.50 \text{ mV}) \cdot (44.281)^2 \left(\frac{1}{\sqrt{1 + \left(\frac{2600}{150} \right)^2}} \right)^2 (0.99089)^2 = \underline{\underline{1.668 \text{ mV}}}$$

• Thus, $SNR_{out} = \left(\frac{|V_{signal}|_{out}}{|V_{noise}|_{out}} \right)^2 = \left(\frac{4500 \text{ mV}}{1.668 \text{ mV}} \right)^2 = 7.28 \times 10^6$

or $SNR_{dB, out} = 20 \log \left(\frac{4500}{1.668} \right) = \boxed{68.6 \text{ dB} = SNR_{dB, out}}$

★ much better SNR !